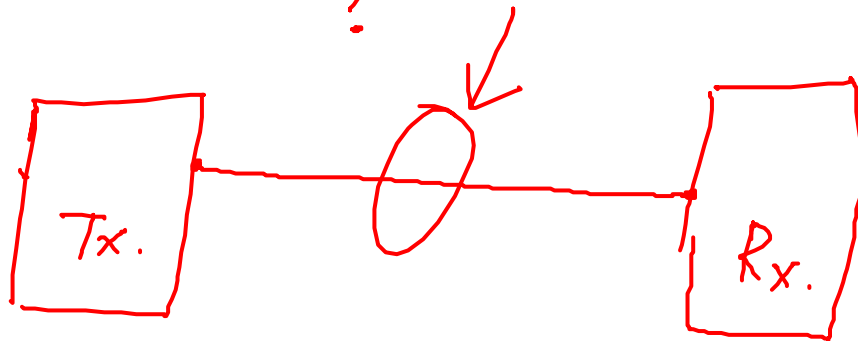


Unit - I

Introduction to Electricity

Dr.Santhosh.T.K.

✓
Wireless power transmission




Enrod

UNIT – I

10 Periods


- > **Introduction and Basic Concepts:** Concept of Potential difference, voltage, current - Fundamental linear passive and active elements to their functional current-voltage relation - Terminology and symbols in order to describe electric networks - Concept of work, power, energy and conversion of energy- Principle of batteries and application.
- > **Principles of Electrostatics:** Electrostatic field - electric field intensity - electric field strength - absolute permittivity - relative permittivity - capacitor composite – dielectric capacitors - capacitors in series & parallel - energy stored in capacitors - charging and discharging of capacitors.

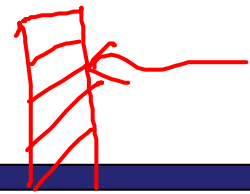- Charge is *conserved*: it is neither created nor destroyed
- Symbol: Q or q ; units are coulomb (C)
- The smallest charge, the *electronic charge*, is carried by an electron (-1.602×10^{-19} C) or a proton ($+1.602 \times 10^{-19}$ C)
- In most circuits, the charges in motion are electrons




Current is the rate of charge flow:

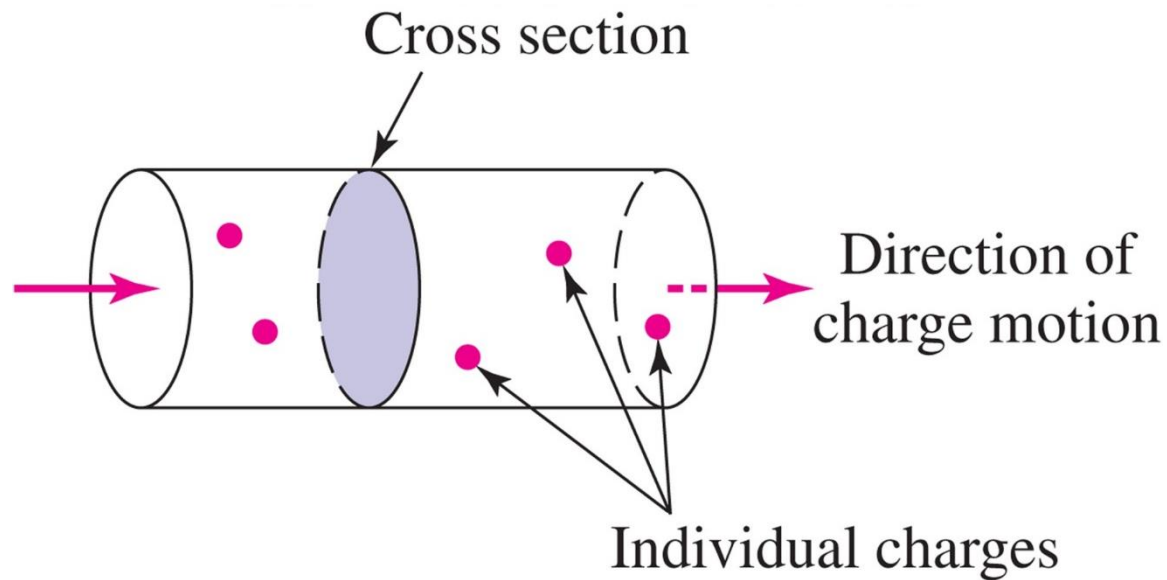1 ampere = 1 coulomb/second (or $1 \text{ A} = 1 \text{ C/s}$)



Current-Water Analogy


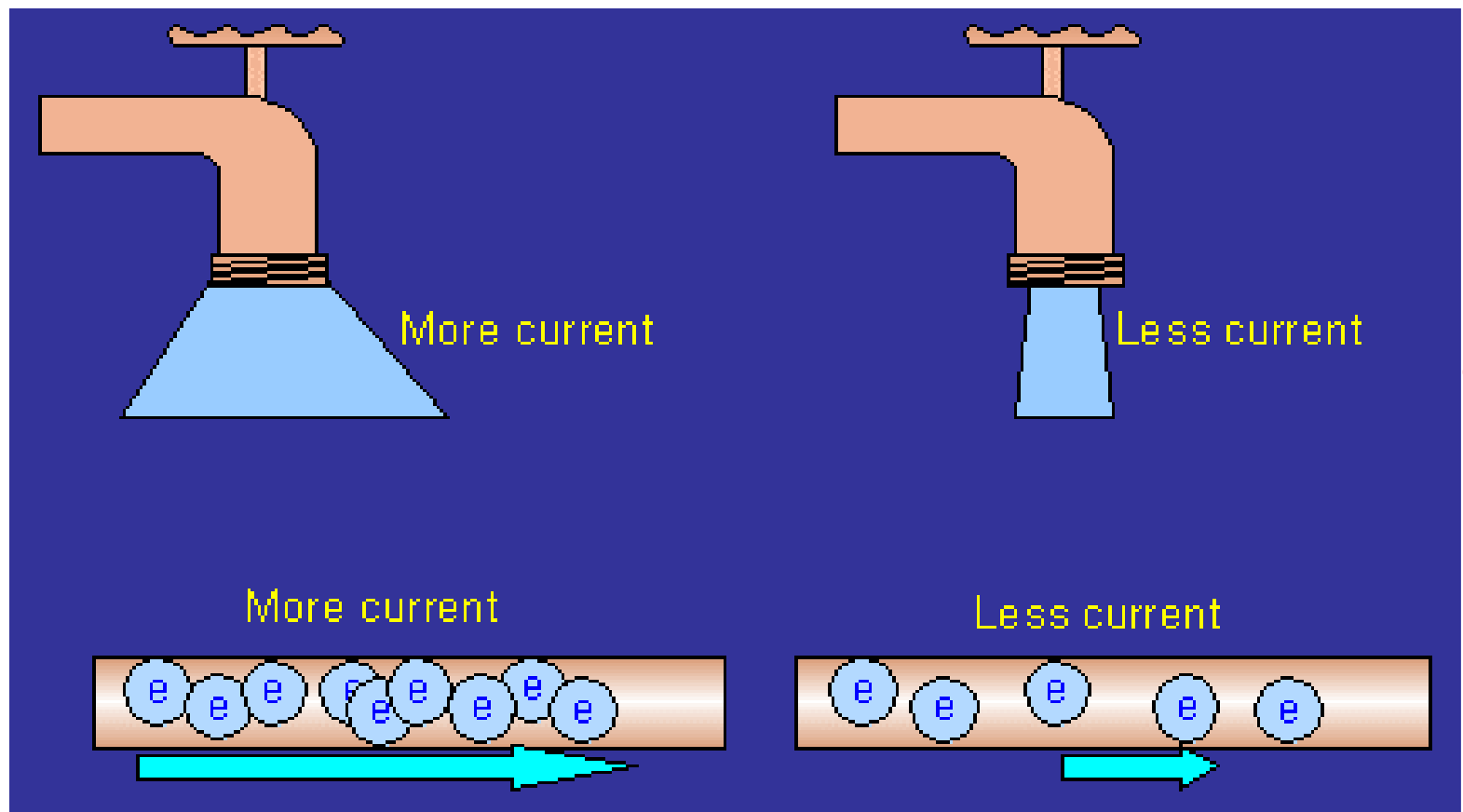


Voltage

• Symbol: V

• Unit: Volt

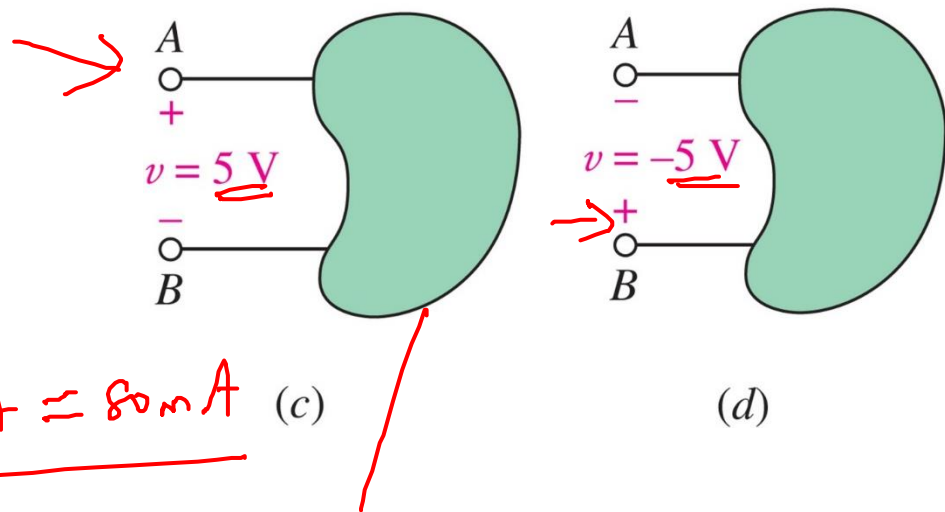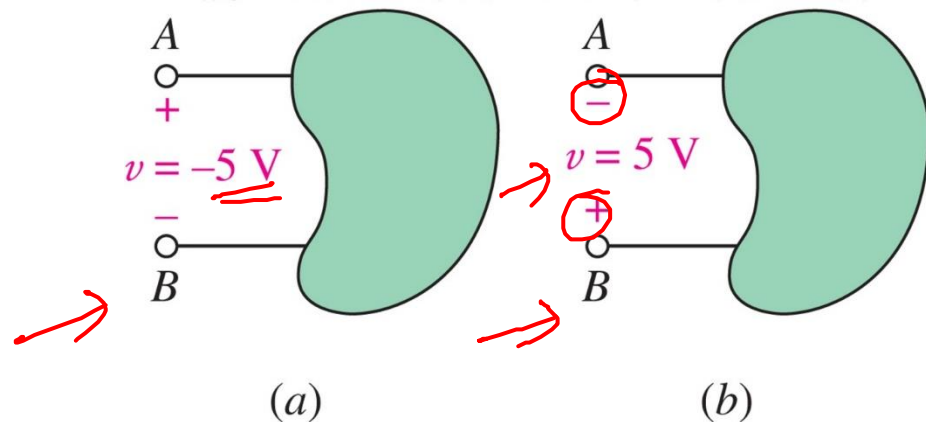- Potential difference across two terminals in a circuit “across variable.”
- In order to move charge from point A to point B, work needs to be done.
- Like potential energy at a water fall.




A

B

Voltage-Water Analogy


1 ϕ \rightarrow 230V, 50Hz \rightarrow IND
 \rightarrow 110V, 60Hz \rightarrow NA

1 ϕ
3 ϕ

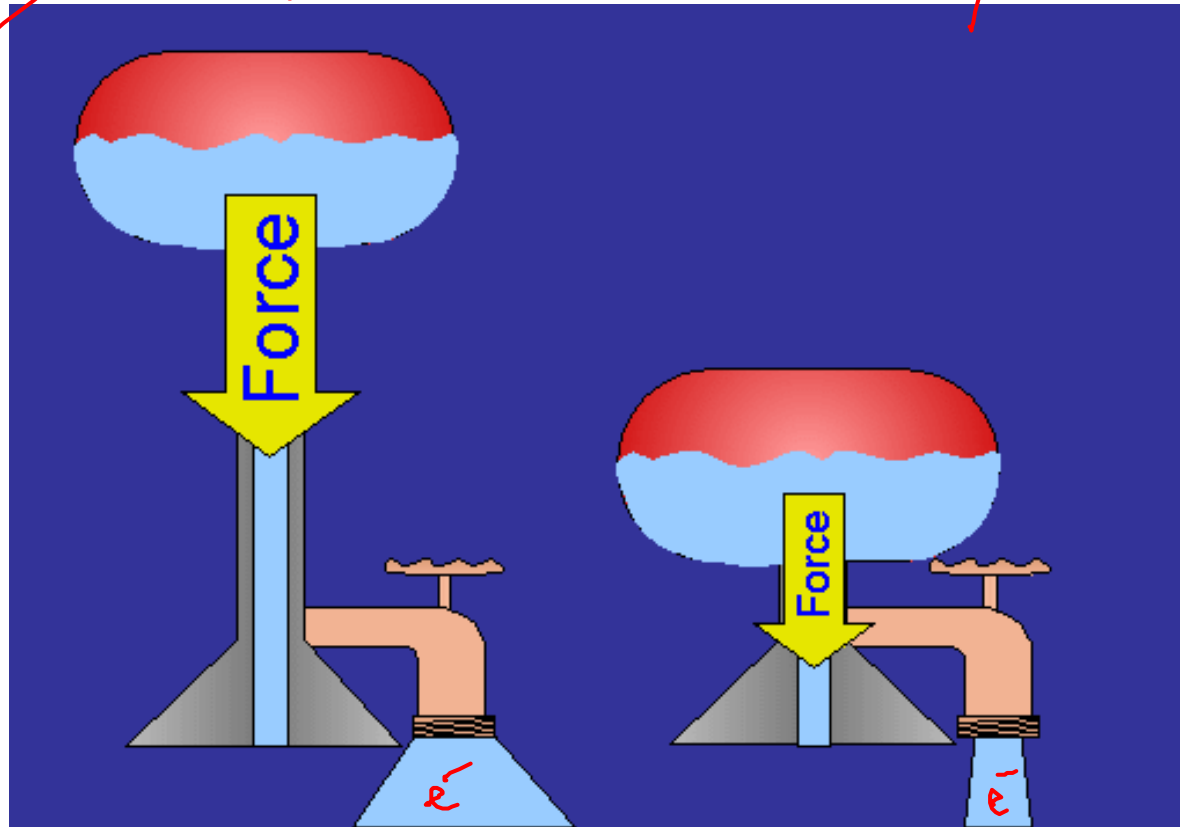


Voltage/Current-Water Analogy


Electrical System

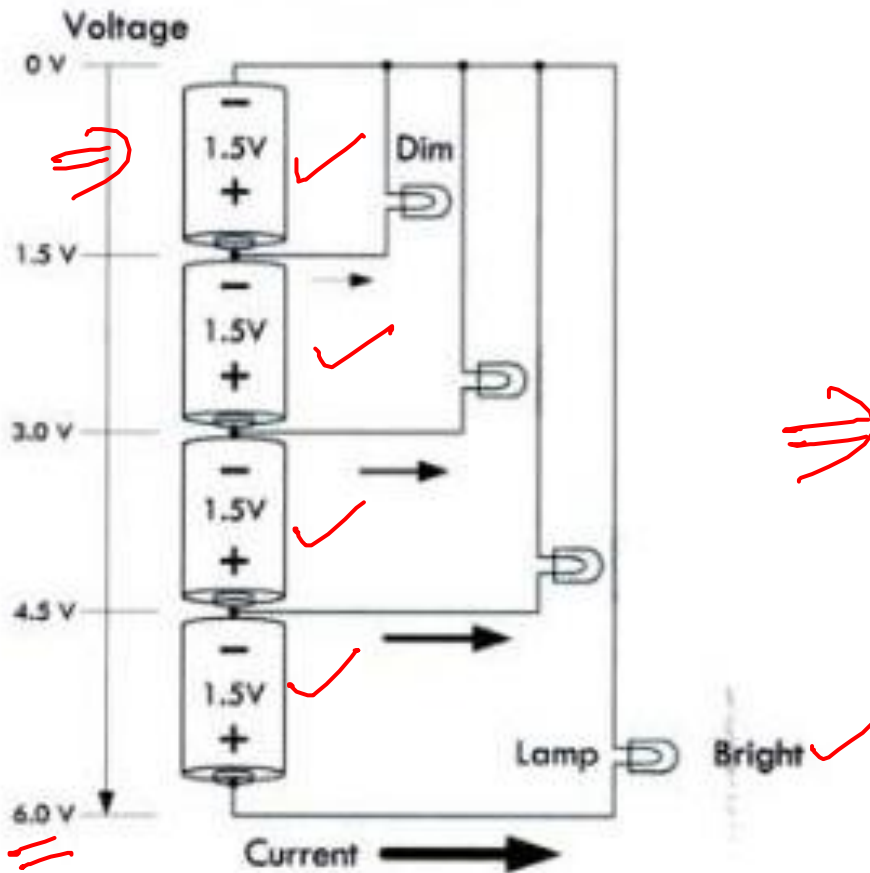

Water System

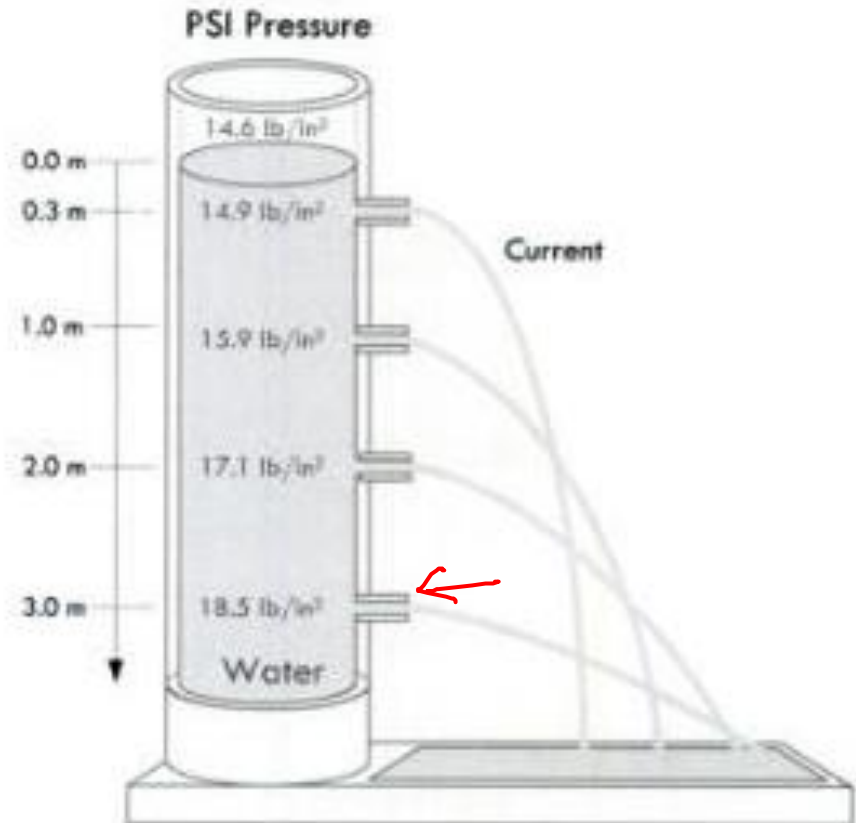


Series Connection

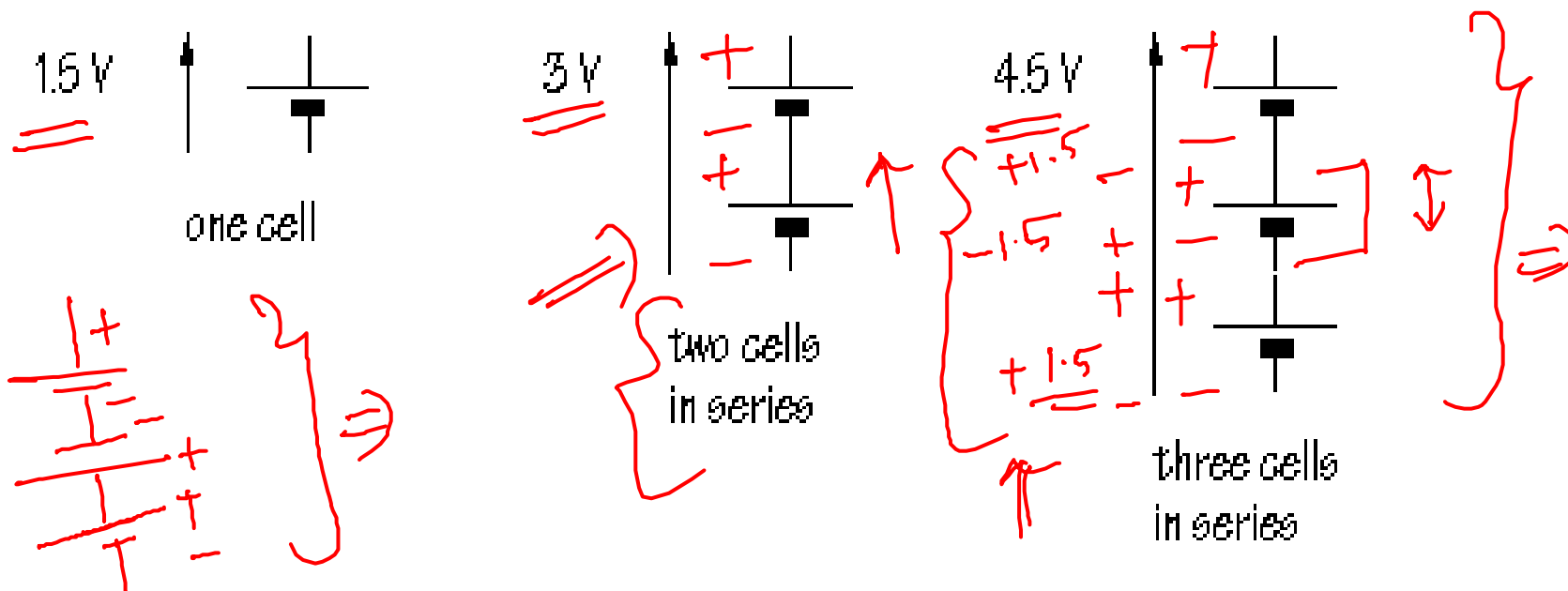

- Each cell provides 1.5 V
- Two cells connected one after another, **in series**, provide 3 V , while three cells would provide 4.5 V
- Polarities matter

Parallel Connection

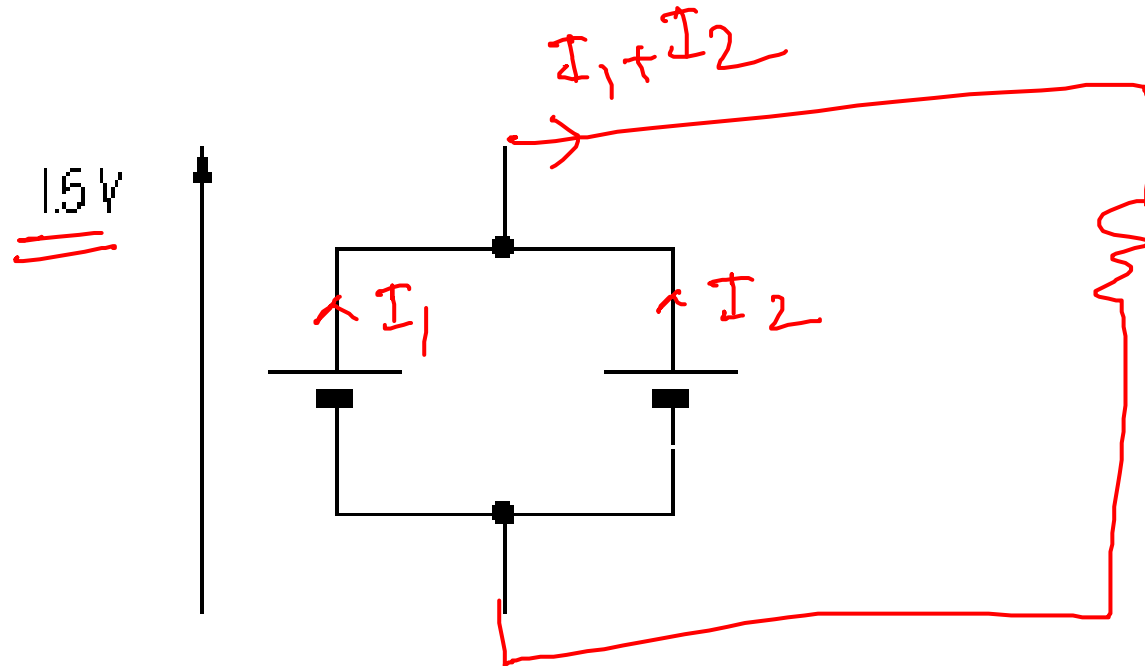


- If the cells are connected in parallel, the voltage stays at 1.5 V, but now a larger current can be drawn.

Power: $p = v i$

The power required to push a current i (C/s) into a voltage v (J/C) is $p = vi$ (J/s = W).


When power is positive, the element is *absorbing* energy.

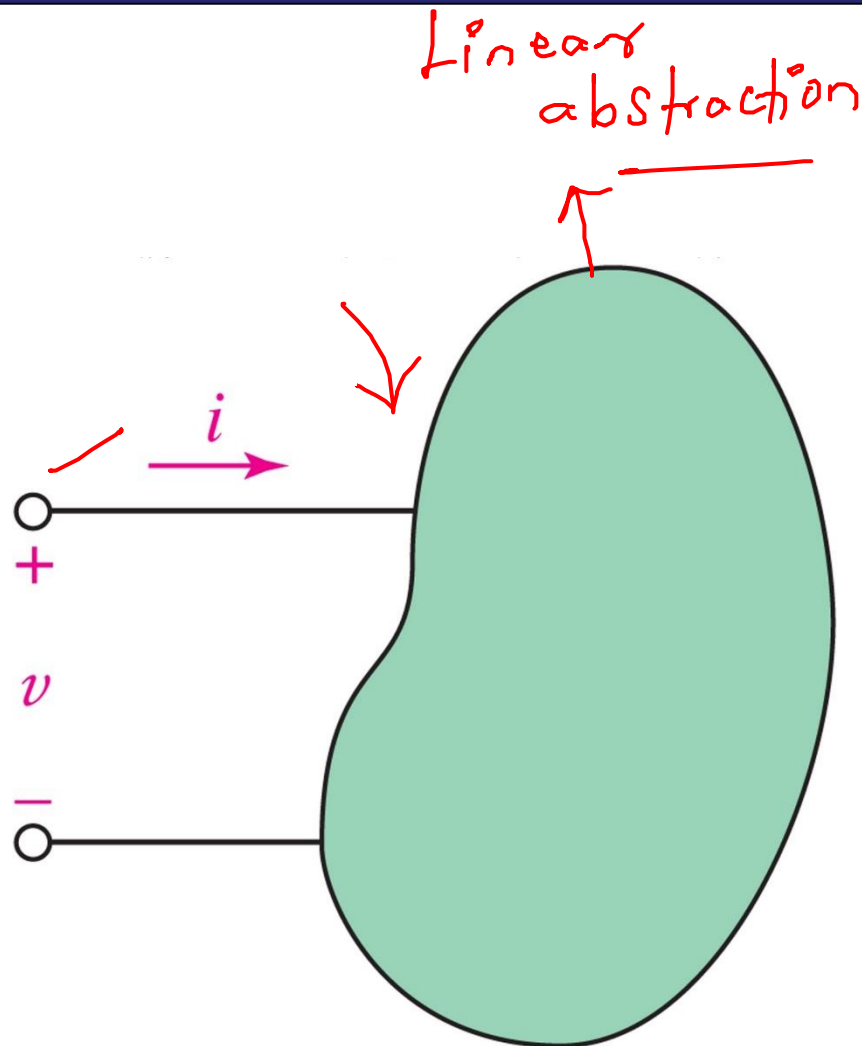When power is negative, the element is *supplying* energy.




Example: Power

$$2 \times 3 = 6 \text{ W}$$

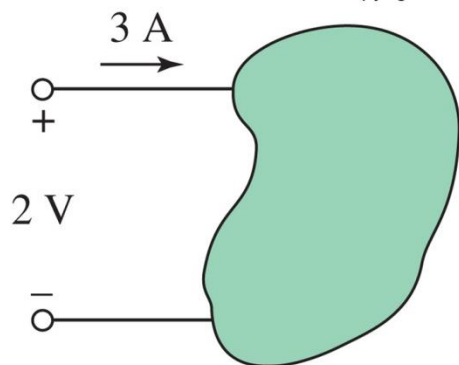


(a)

$$-2 \times -3 = 6 \text{ W}$$

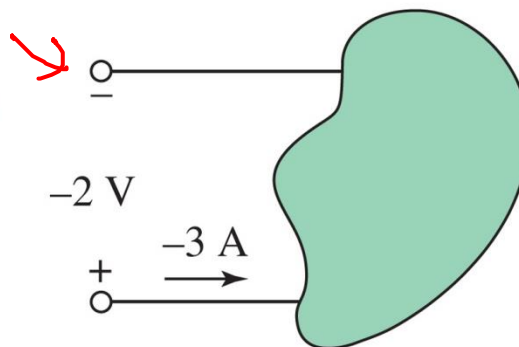

(b)

$$+4 \times -5 = -20 \text{ W}$$

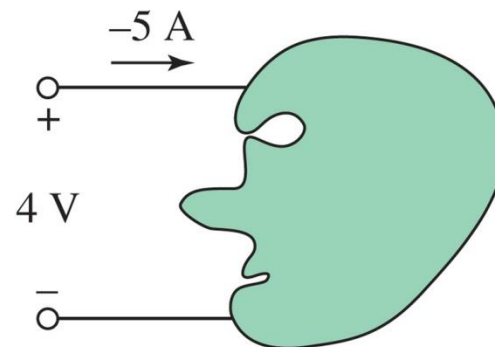

(c)

How much power is absorbed by the three elements above?


$$P_a = +6 \text{ W}, P_b = +6 \text{ W}, P_c = -20 \text{ W}.$$

(Note: (c) is actually supplying power)


R L C

Resistance

Linear circuit abstraction




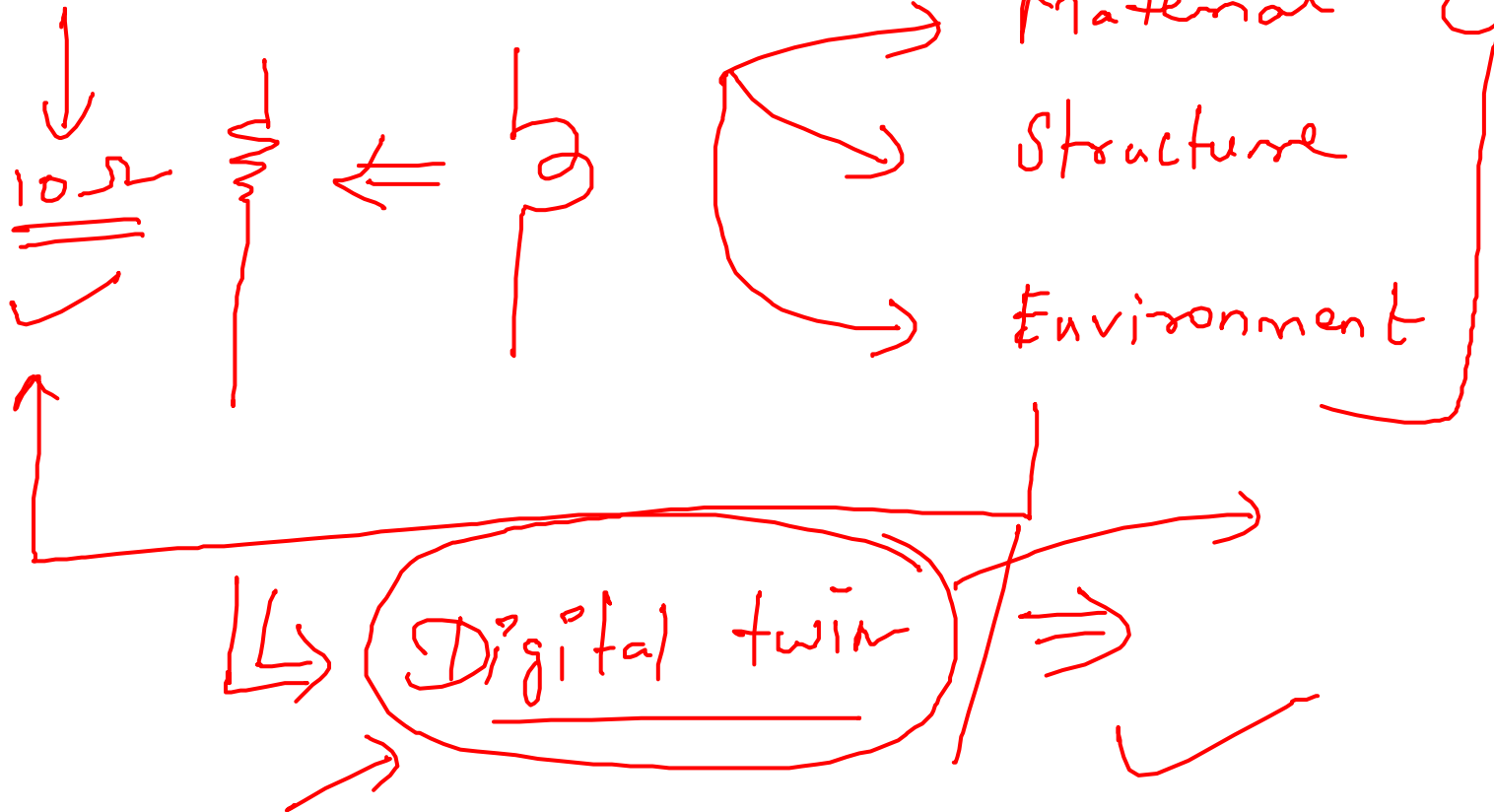


Wire-Water Analogy

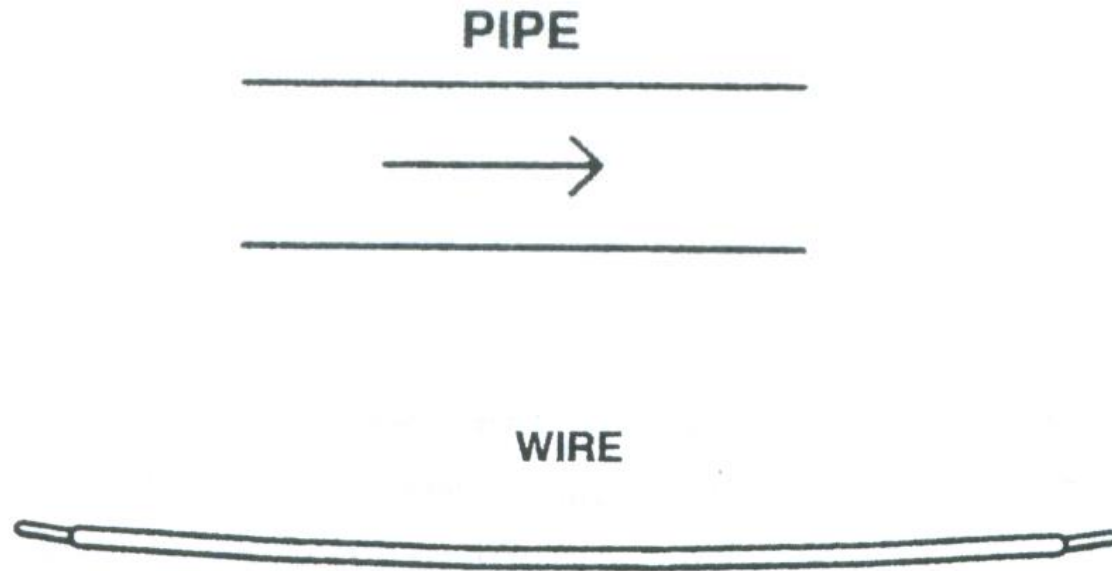

Resistors-Water Analogy

ROCKS IN THE PIPE

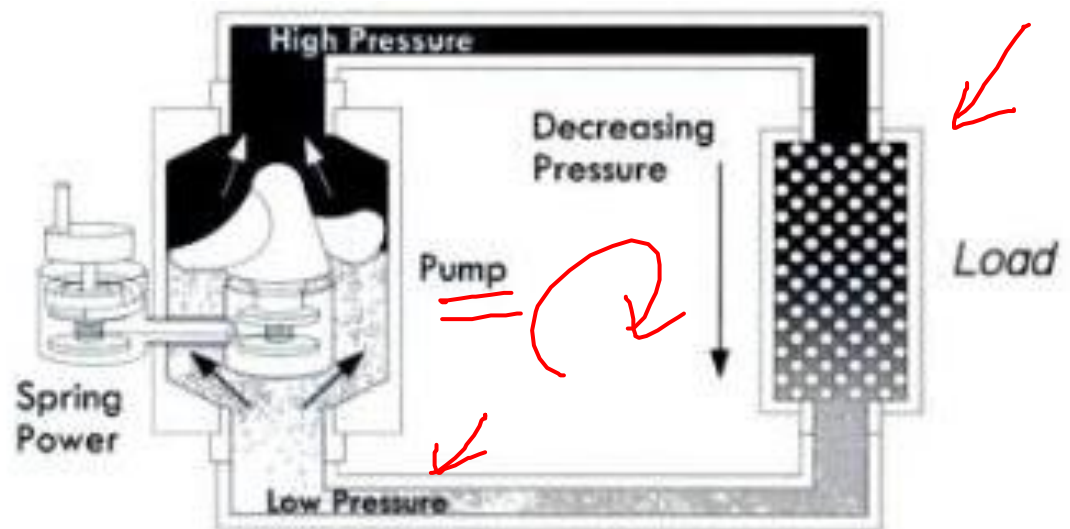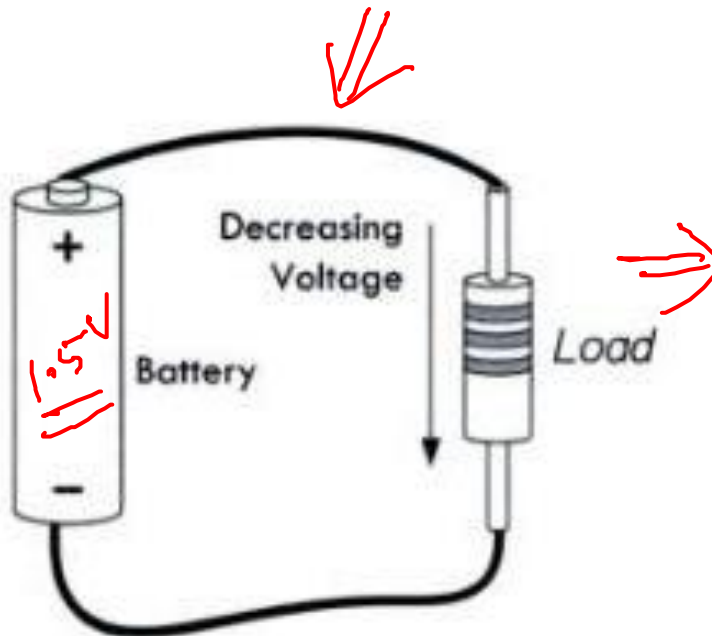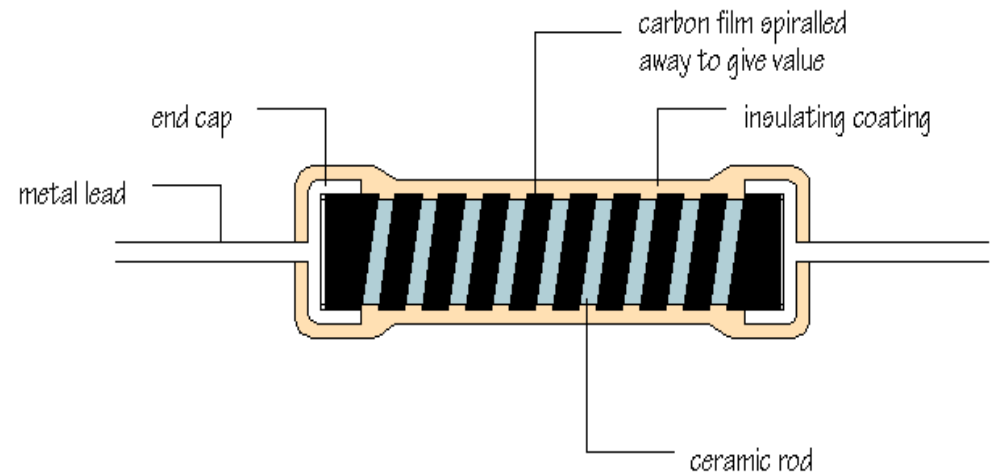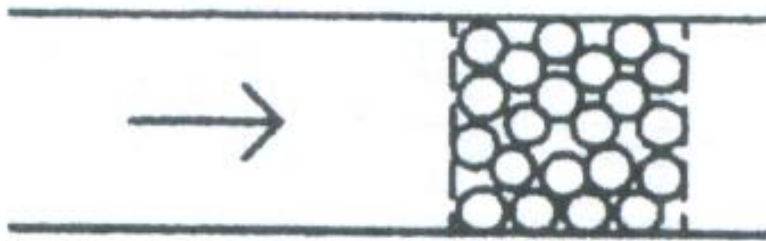

Resistor V-I Characteristic

- In a typical resistor, a conducting element displays linear voltage-current relationship. (i.e., current through a resistor is directly proportional to the voltage across it).

$$I \propto V$$

- Using G as a constant of proportionality, we obtain:

$$I = GV$$


- Equivalently,

$$V = RI \text{ (or } V = IR)$$

where $R = 1/G$.

- R is termed as the resistance of conductor (ohm, Ω)
- G is termed as the conductance of conductor (mho, \mathfrak{U})


Variable Resistor: Rotary Potentiometers

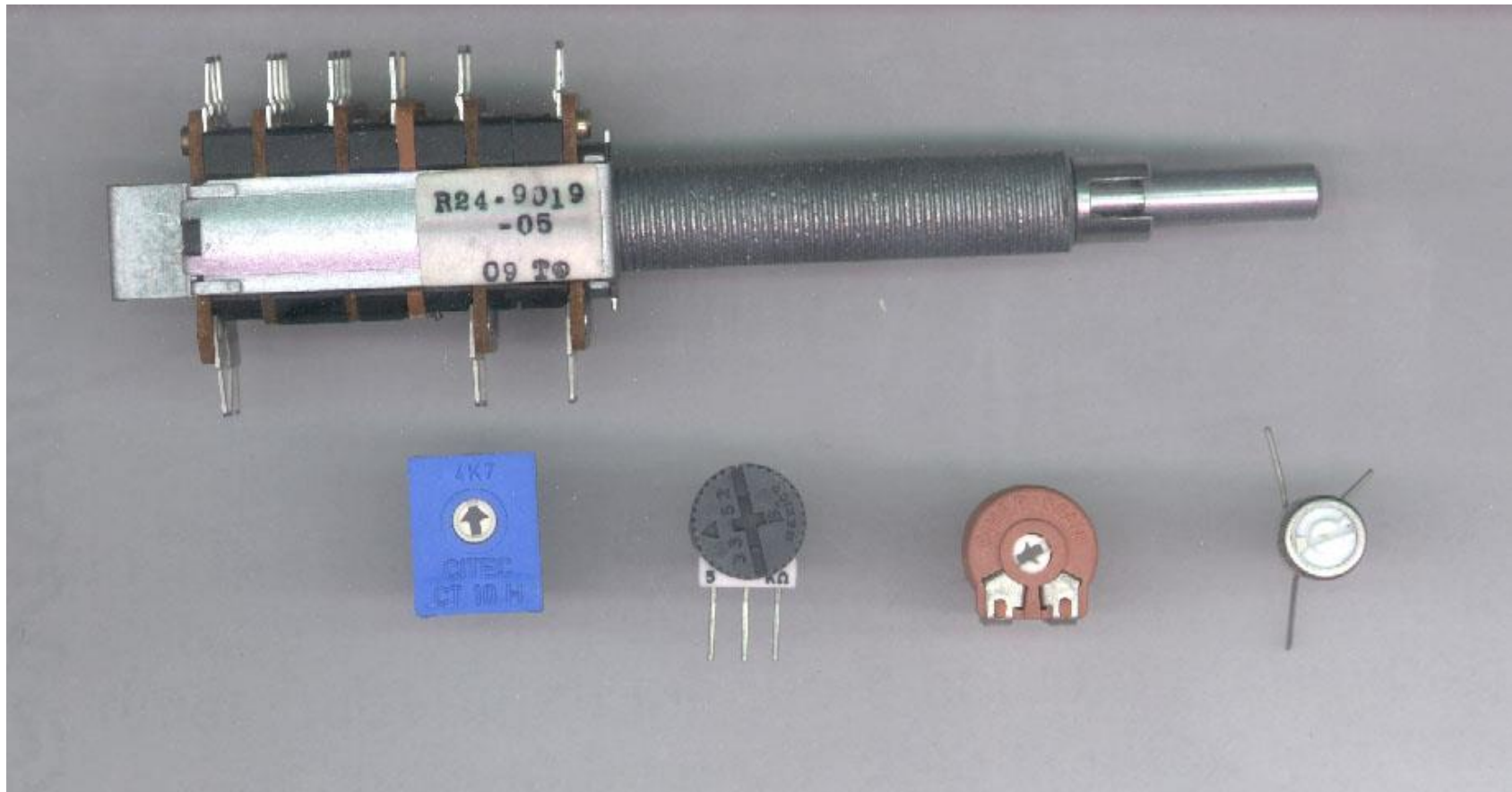

Variable Resistor: Other Examples






Photoresistor

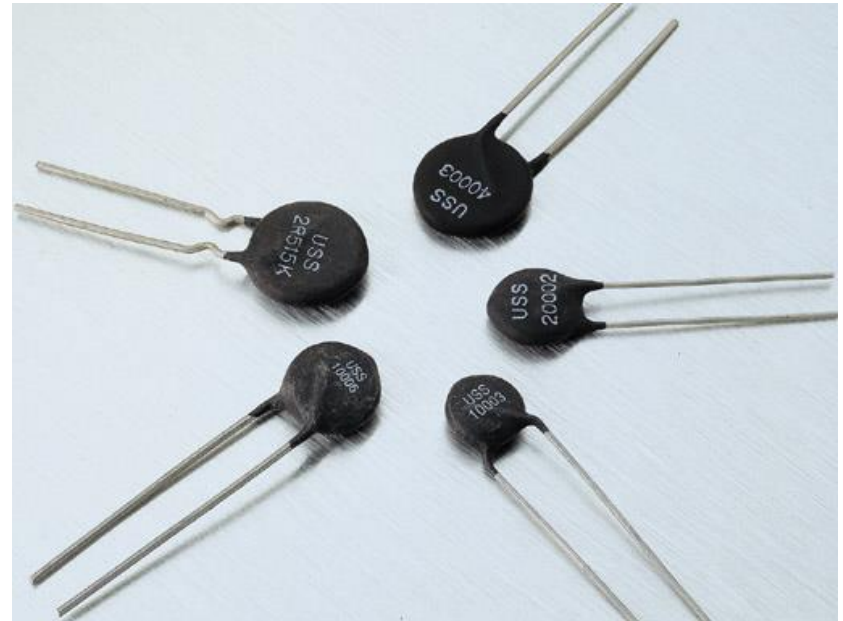


Thermistor

Resistor Examples

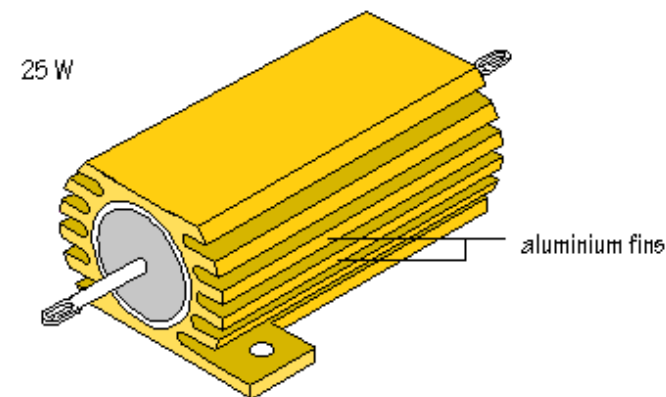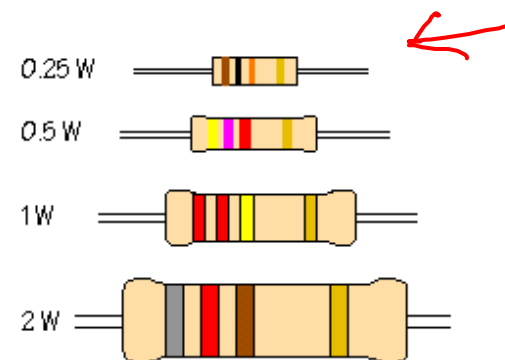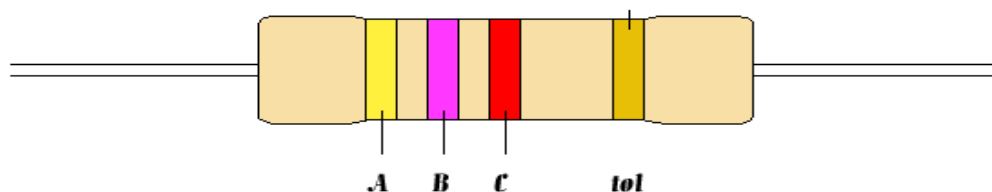Resistor value = $AB \times 10^C \pm tol\% (\Omega)$




Resistors in Series

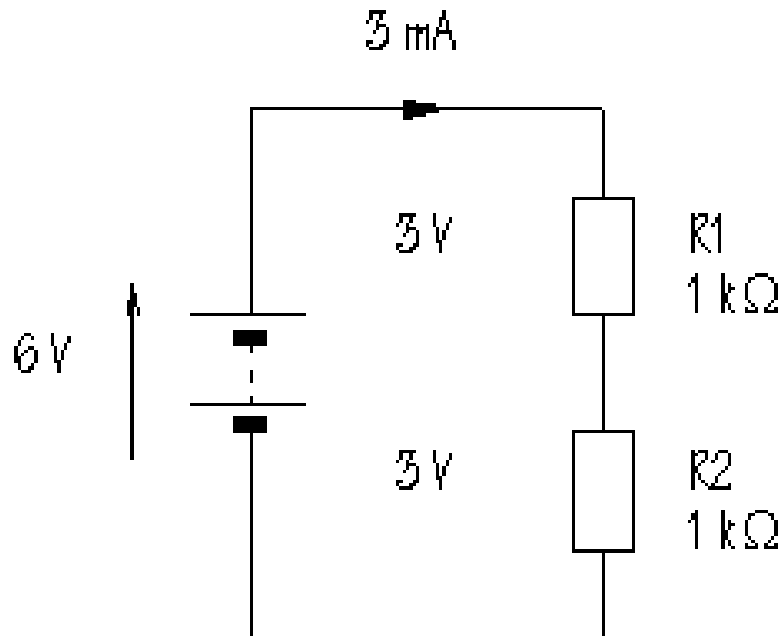

$$R_{\text{total}} = R_1 + R_2$$

$$R_{\text{total}} = 1 + 1 = 2\text{k}\Omega$$


Resistors in Parallel

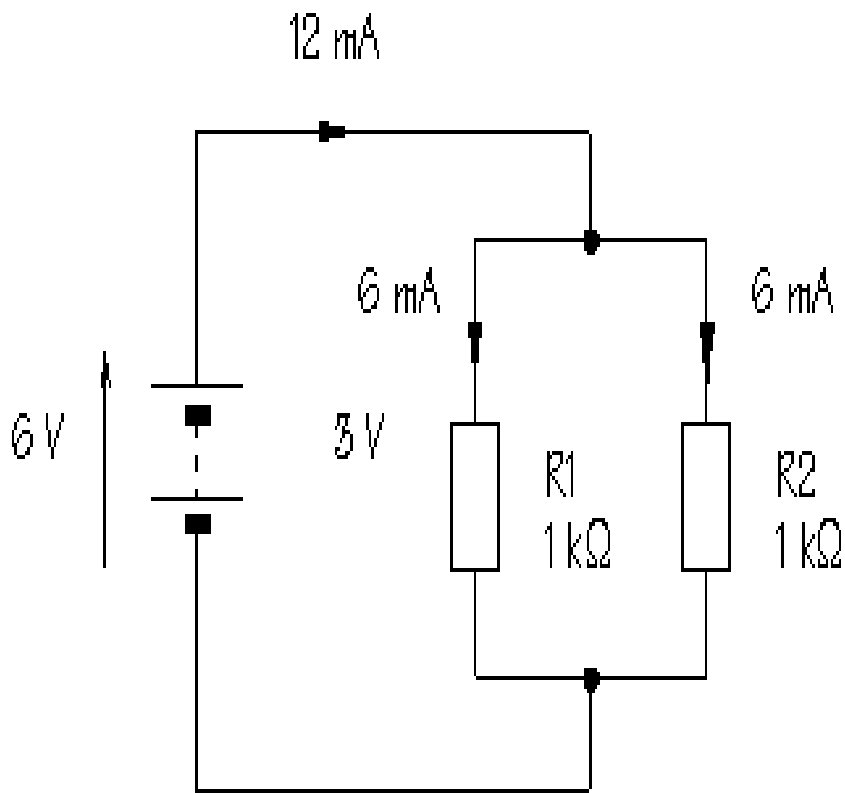

$$R_{total} = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$R_{total} = \frac{1 \times 1}{1 + 1} = \frac{1}{2} = 0.5 k\Omega$$


Exercise 1

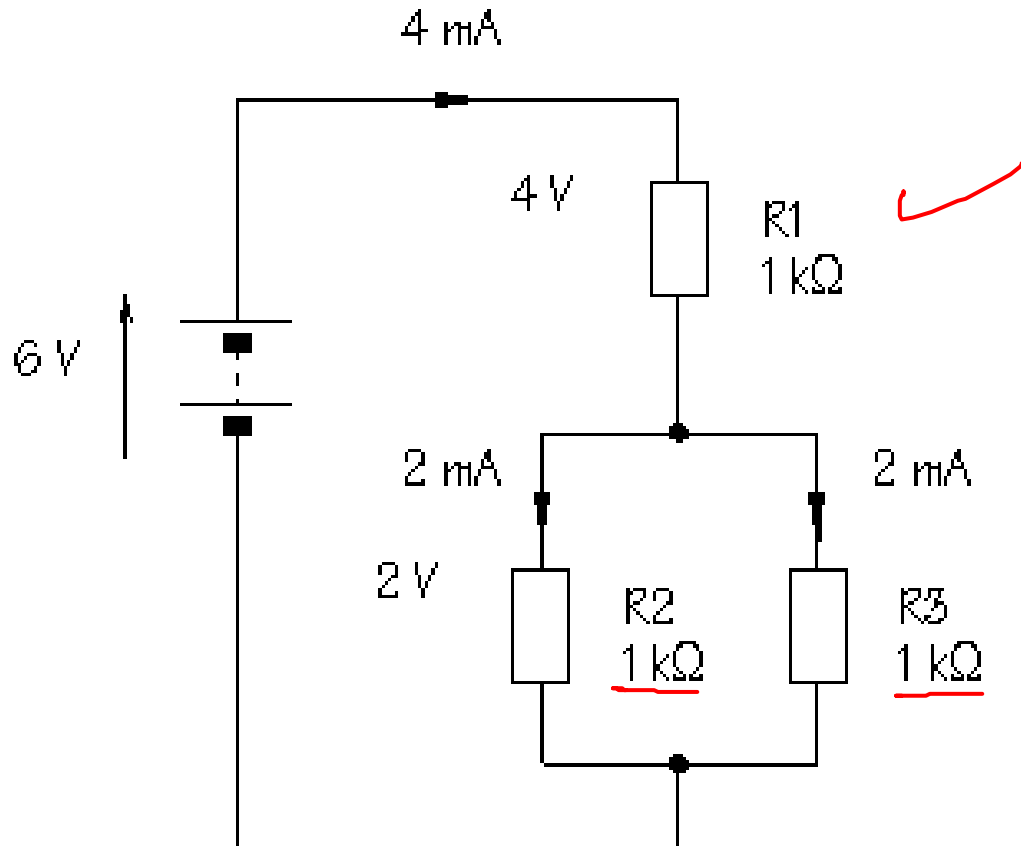

$$R_{total} = R_1 + \frac{R_2 \times R_3}{R_2 + R_3}$$



$$R_{total} = 1 + \frac{1 \times 1}{1 + 1} = \frac{3}{2} = \underline{\underline{1.5 k\Omega}}$$

Voltmeter Connection

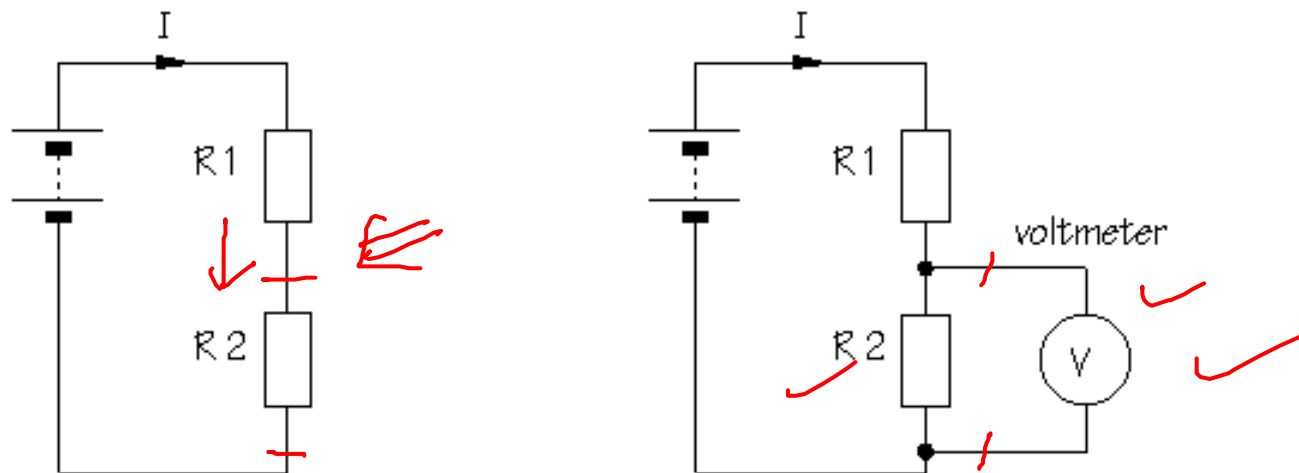


- The voltmeter is connected in parallel between two points of circuit
- A voltmeter should have a very **HIGH** input impedance

Ammeter Connection

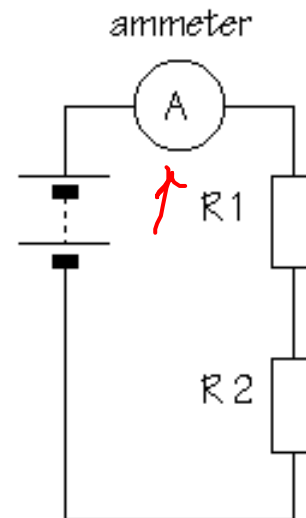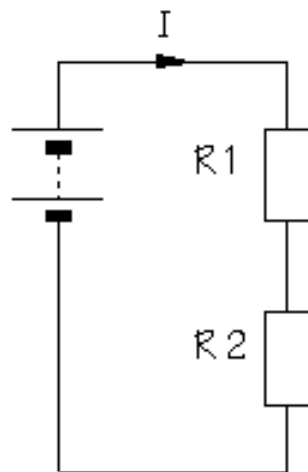


- Break the circuit so that the ammeter can be connected in series
- All the current flowing in the circuit must pass through the ammeter
- An ammeter must have a very **LOW** input impedance

Capacitor Symbols

 

**Fixed
capacitor**

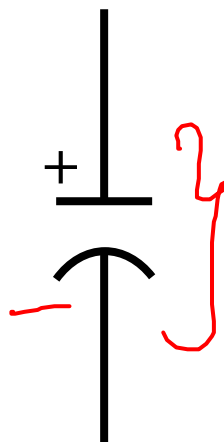


**Polarized
capacitor**





**Variable
capacitor**

Capacitor Water Pipe Analogy

- Water capacitor: a tube with a rubber membrane in the middle
- Rubber membrane analogous to the dielectric, two chambers analogous to two capacitor plates
- When no water pressure is applied on the water capacitor, the two chambers contain same amount of water (uncharged)
- When pressure is applied on the top chamber, the membrane is pushed down causing the water to be displaced from the bottom chamber (appearance of current flow → displacement current)

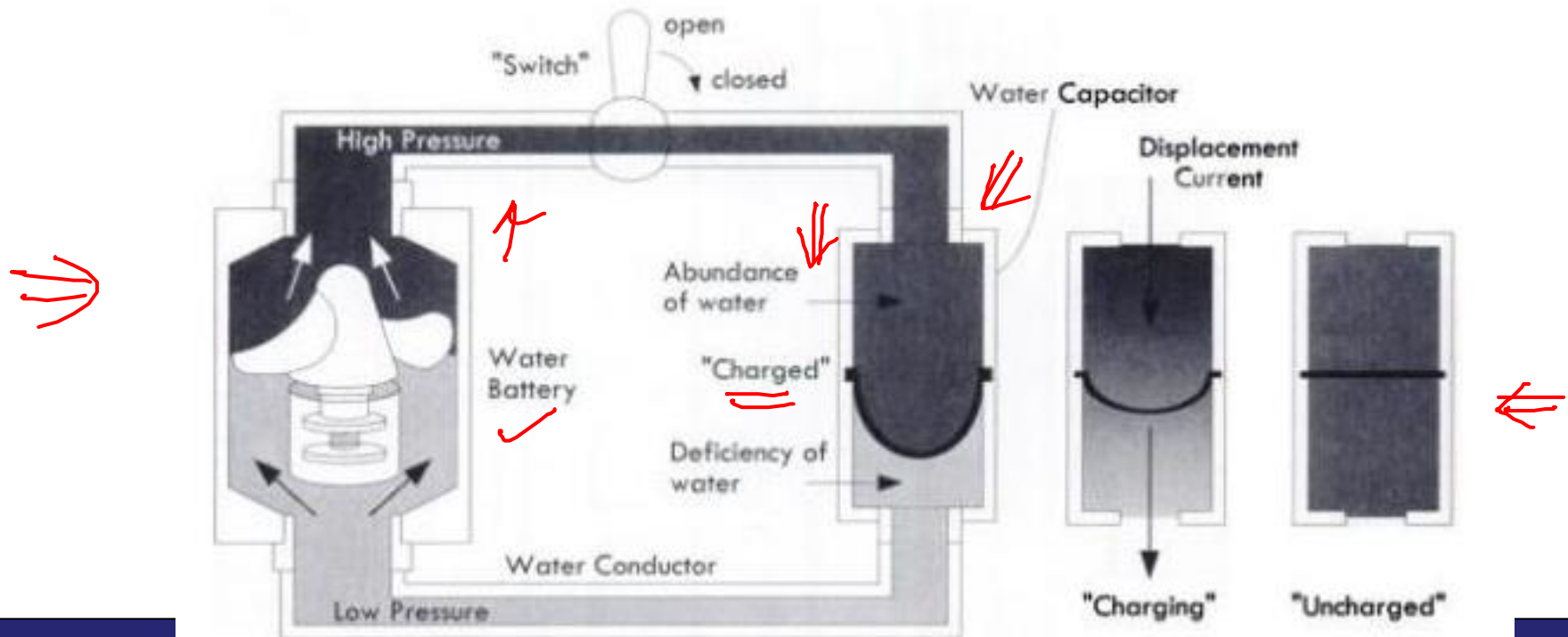

Capacitor Variations

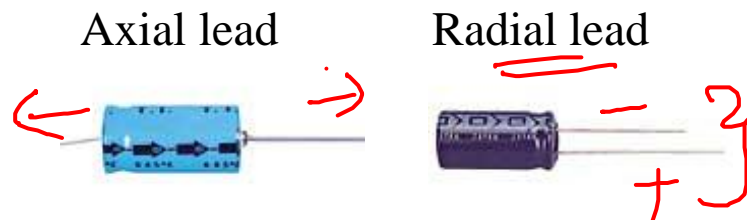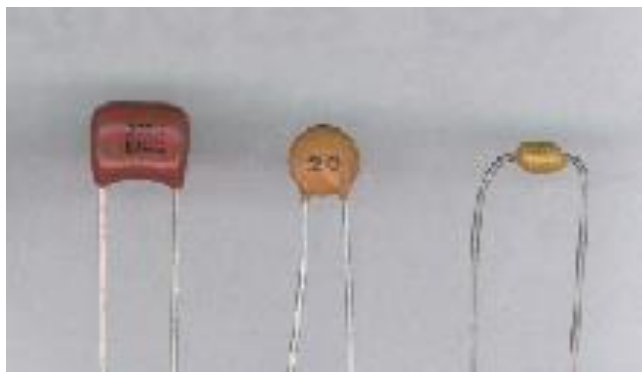

•Electrolytic

- Aluminum, tantalum electrolytic
- Tantalum electrolytic capacitor has a larger capacitance when compared to aluminum electrolytic capacitor
- Mostly polarized.
- Greater capacitance but poor tolerance when compared to nonelectrolytic capacitors.
- Bad temperature stability, high leakage, short lives

•Ceramic capacitors


- very popular nonpolarized capacitor
- small, inexpensive, but poor temperature stability and poor accuracy
- ceramic dielectric and a phenolic coating
- often used for bypass and coupling applications

Capacitor Variations




- Mylar

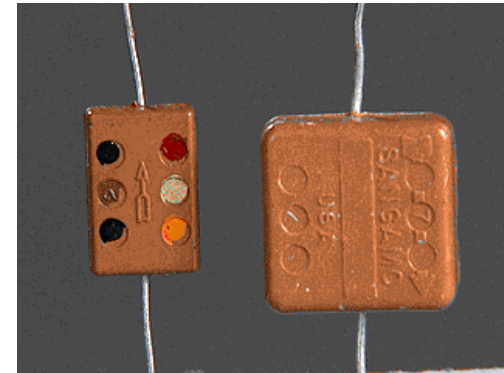- very popular, nonpolarized
- reliable, inexpensive, low leakage
- poor temperature stability



- Mica

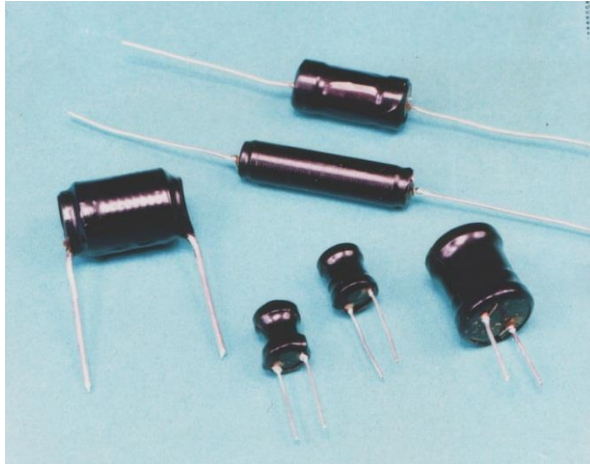- extremely accurate, low leakage current
- constructed with alternate layers of metal foil and mica insulation, stacked and encapsulated
- small capacitance
- often used in high-frequency circuits (i.e. RF circuits)




•Chokes



–general-purpose inductors that act to limit or suppress fluctuating current.

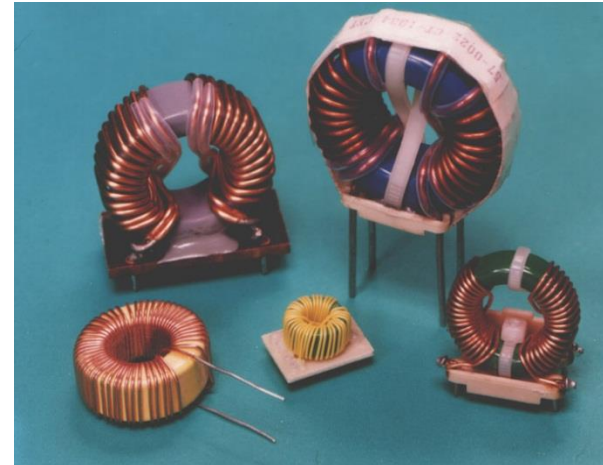–some use a resistor-like color code to specify inductance values.



•Toroidal coil




–resembles a donut with a wire wrapping

–high inductance per volume ratios, high quality factors, self-shielding, can be operated at extremely high frequencies

Open and Short Circuits

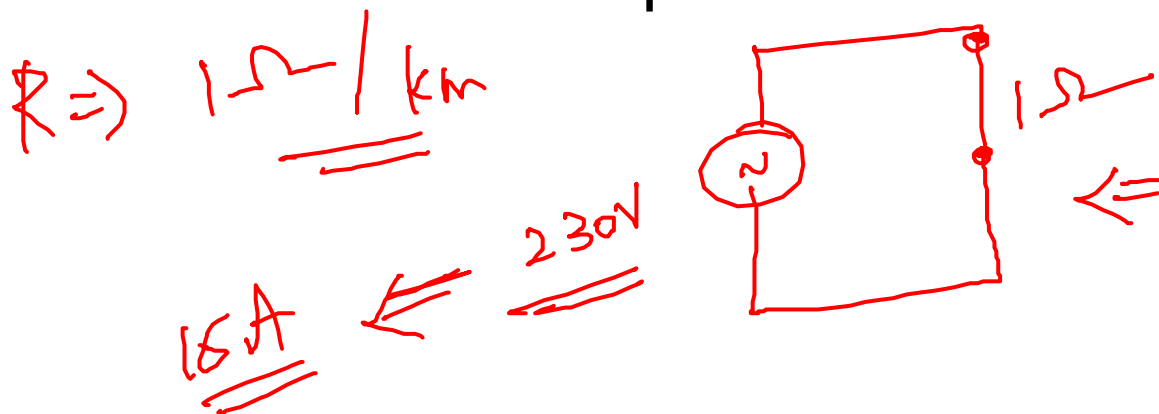- An open circuit between A and B means $i=0$.
- *Voltage across* an open circuit: any value.
- An open circuit is equivalent to $R = \infty \Omega$.
- A short circuit between A and B means $v=0$.
- *Current through* a short circuit: any value.
- A short circuit is equivalent to $R = 0 \Omega$.



Summary

Basics

