

**SASTRA**

DEEMED TO BE UNIVERSITY

THINK DEEPT, THINK TRANSCENDENT, THINK SASTRA

KARNAUGH MAP (K-MAP) :-

The complexity of the digital logic gates that implement a Boolean function is directly related to the complexity of the algebraic expression from which the function is implemented.

* The simplification of Boolean function by algebraic method is tedious because it lacks specific rules to predict each succeeding step in the manipulative process.

* The K-map method provides a straight forward procedure for simplifying or minimizing the

**SASTRA**

DEEMED TO BE UNIVERSITY

THINK DEEPT, THINK TRANSCENDENT, THINK SASTRA



Boolean function.

- * This method was first proposed by Veitch and modified by Karnaugh.
- * This method is also called as Veitch diagram.
- * This method provides a pictorial representation of all possible ways a function may be expressed in a standard form.



- * Each square represents one minterm.
- * Any two adjacent squares in the map differ by only one variable which is primed in one square and unprimed in the other.
- * Minterms are not arranged in a binary sequence but in a sequence



$$m_0 + m_2$$



- * Each square represents one minterm. $\rightarrow x'y \rightarrow x'y, x'y, xy, xy$
- * Any two adjacent squares in the map differ by only one variable which is primed in one square and unprimed in the other.
- * Minterms are not arranged in a binary sequence but in a sequence

$$\begin{matrix} x'y \\ x'y \\ x'y \\ x'y \\ x'y \\ x'y \\ x'y \\ x'y \end{matrix}$$



in which only one bit changes from
0 to 1 or 1 to 0.

Two - Variable map :-

x \ y	0	1
0	m_0	m_1
1	m_2	m_3

$m_0 - 00$
 $m_1 - 01$
 $m_2 - 10$
 $m_3 - 11$



Three - Variable map :-

x \ yz	00	01	11	10
0	m_0	m_1	m_3	m_2
1	m_4	m_5	m_7	m_6

10
000
00
 $x' y' z'$
 $x' y' z$

000
001



Four-Variable map :-

yz \ wx	00	01	11	10
00	m_0	m_1	m_3	m_2
01	m_4	m_5	m_7	m_6
11	m_{12}	m_{13}	m_{15}	m_{14}
10	m_8	m_9	m_{11}	m_{10}

$$m_0 \rightarrow m_1, m_4, m_2, m_8$$

$$m_4 \rightarrow m_0, m_5, m_6, m_{12}$$

$$m_{15} \rightarrow m_7, m_{13}, m_9, m_{11}$$

Problems :- $f(x, y) = x'y' + x'y + xy'$
① Simplify $f(x, y) = \Sigma(0, 1, 2)$

x \ y	0	1
0	1	1
1	1	0

$$f(x, y) = x'y' + x'y + xy'$$

$$f(x, y) = y' + x'$$

$$\therefore f(x, y) = x' + y'$$

$$\begin{aligned} &= x' \cdot (y' + y) + xy' \\ &= x' \cdot 1 + xy' \\ &= x' + xy' \\ &= (x' + x) \cdot (x' + y') \\ &= x' + y' \end{aligned}$$

