

# Unit - I

## 1.8 Capacitors

**Dr.Santhosh.T.K.**

CSP - Concentrating Solar-Thermal Power

Batteries

2017 → Zunum Aero

Eviation

↳ Alice

68

6

100 Vs 1100

↓  
 Velis  
Electro

Solar PV

↓  
 ? → Storage

Solar Thermal

S

## UNIT – I

10 Periods


**Introduction and Basic Concepts:** Concept of Potential difference, voltage, current - Fundamental linear passive and active elements to their functional current-voltage relation - Terminology and symbols in order to describe electric networks - Concept of work, power, energy and conversion of energy- Principle of batteries and application.

**Principles of Electrostatics:** Electrostatic field - electric field intensity - electric field strength - absolute permittivity - relative permittivity - capacitor composite – dielectric capacitors - capacitors in series & parallel - energy stored in capacitors - charging and discharging of capacitors.
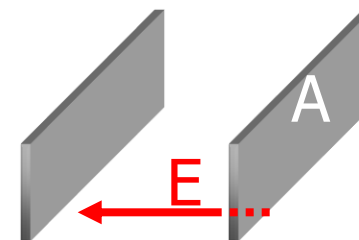
# Capacitors: the basics

What is a capacitor?  $\rightarrow \Phi_{ans}$   
 $\rightarrow \underline{TV}$

- device for **storing charge**
- simplest example: two parallel conducting plates separated by air



$V_0$   $\xleftarrow{d}$   $V_1$



assortment of  
capacitors

How much charge can a capacitor store?

*/ Supercapacitors*

**Better question:** How much charge can a capacitor store per voltage?

**Capacitance:**  $C = \frac{Q}{V}$

V is really  $|\Delta V|$ , the potential difference across the capacitor

capacitance C is a **device property**, it is always positive

unit of C: farad (F) *↖*

1 F is a large unit, most capacitors have values of C ranging from picofarads to microfarads (pF to  $\mu\text{F}$ ).


micro  $\Rightarrow 10^{-6}$ , nano  $\Rightarrow 10^{-9}$ , pico  $\Rightarrow 10^{-12}$  (Know for exam!)

# Capacitance of parallel plate capacitor

electric field between two parallel charged plates:

$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$$

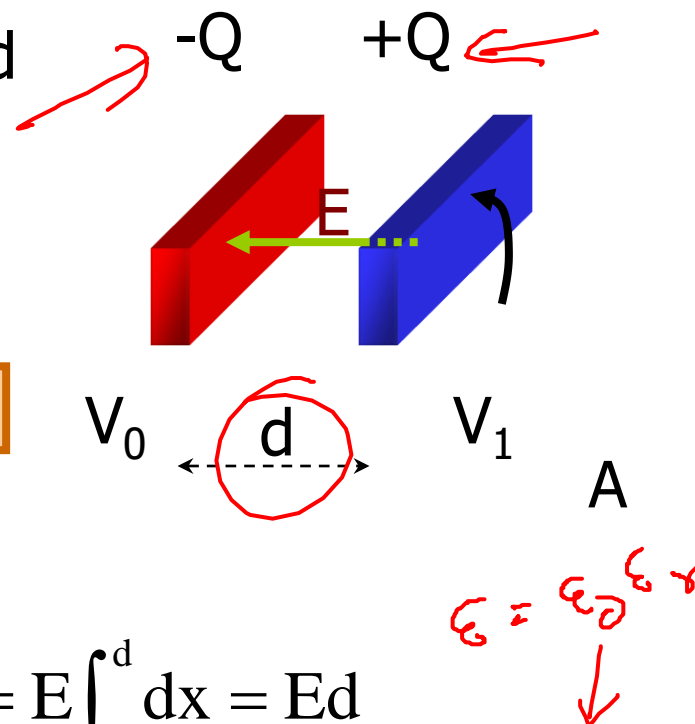Q is magnitude of charge on either plate.



potential difference:

$$\Delta V = V_1 - V_0 = -\int_0^d \vec{E} \cdot d\vec{\ell} = E \int_0^d dx = Ed$$

capacitance:

$$C = \frac{Q}{\Delta V} = \frac{Q}{Ed} = \frac{Q}{\left( \frac{Q}{\epsilon_0 A} \right) d} = \frac{\epsilon_0 A}{d}$$


Example: calculate the capacitance of a capacitor whose plates are 20 cm x 3 cm and are separated by a 1.0 mm air gap.

$$C = \frac{\epsilon_0 A}{d}$$

$$C = \frac{(8.85 \times 10^{-12})(0.2 \times 0.03)}{0.001} \text{ F}$$

$$C = 53 \times 10^{-12} \text{ F}$$

$$C = 53 \text{ pF}$$

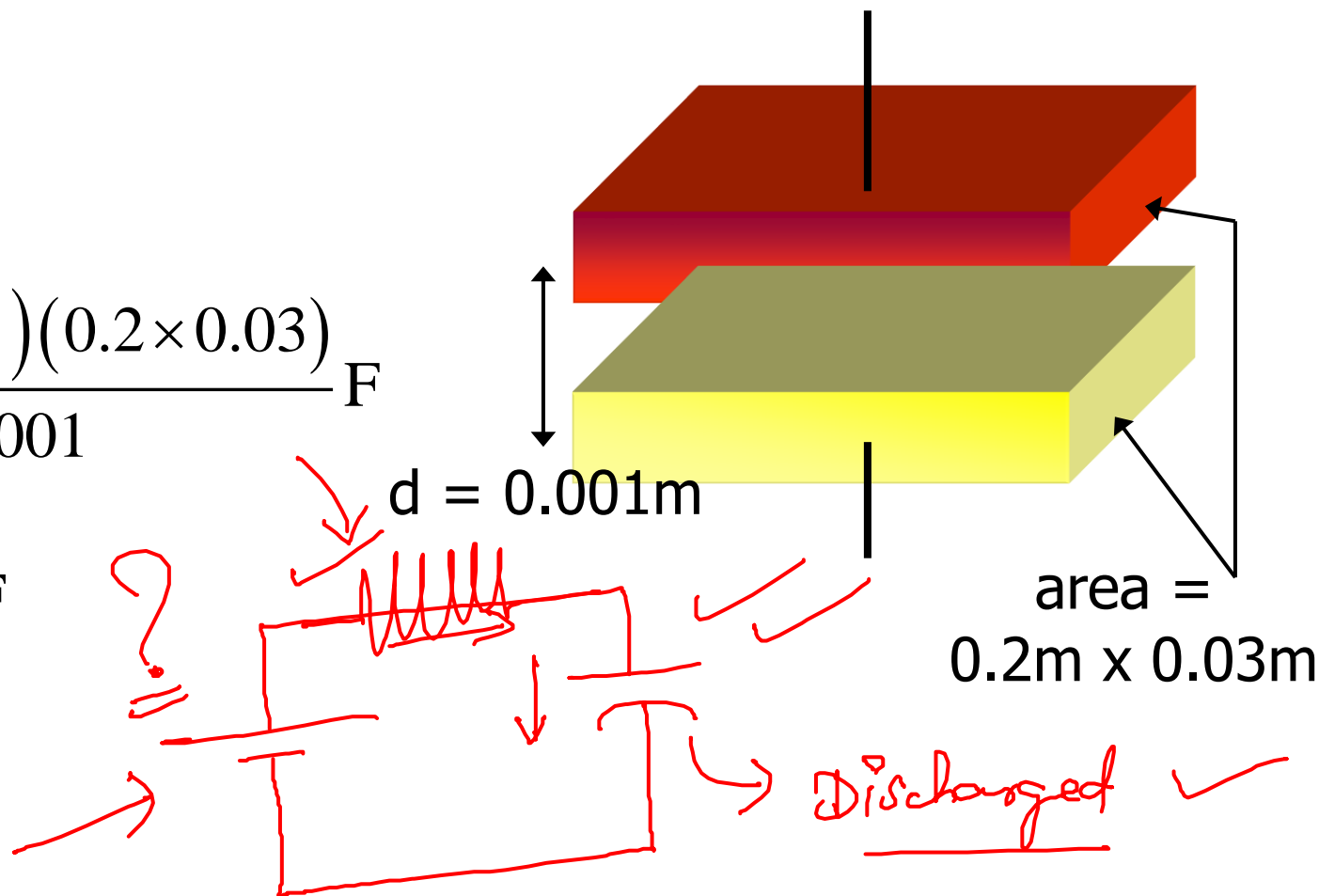


Example: what is the charge on each plate if the capacitor is connected to a 12 volt\* battery?

↓

$$Q = CV$$

$$Q = (53 \times 10^{-12})(12) \text{ C}$$

$$Q = 6.4 \times 10^{-10} \text{ C}$$

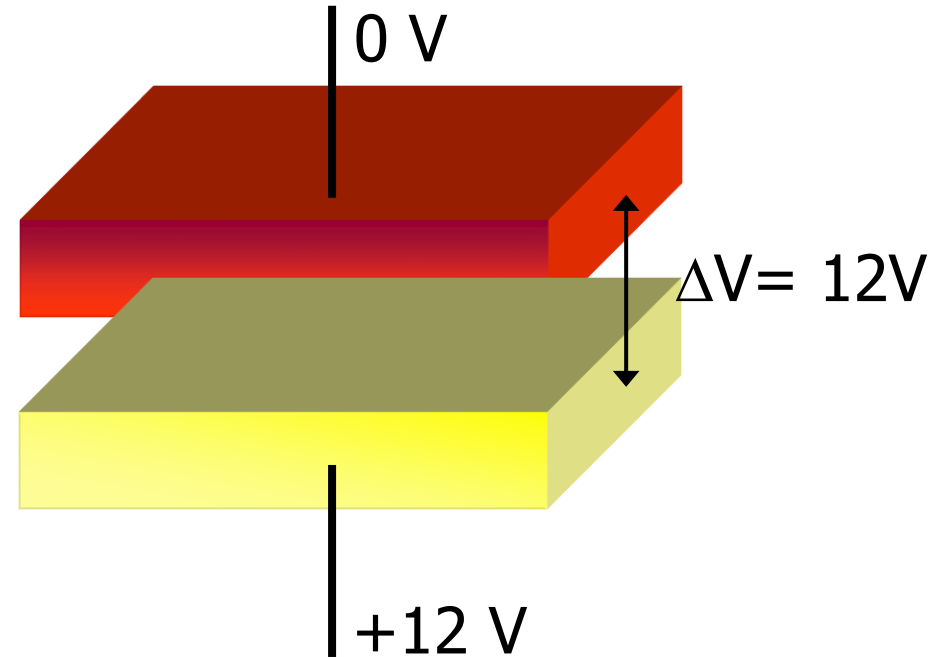

\*Remember, it's the potential difference that matters.




# Example: what is the electric field between the plates?



$$E = \frac{\Delta V}{d}$$

$$E = \frac{12\text{V}}{0.001\text{ m}}$$

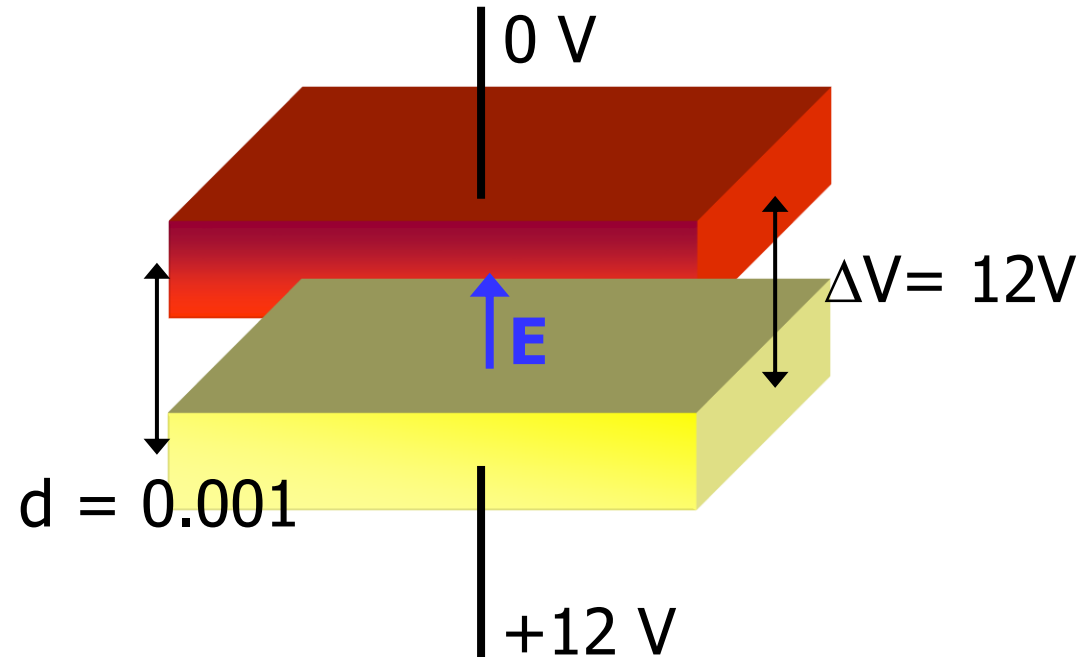
$$\vec{E} = 12000 \frac{\text{V}}{\text{m}}, \text{ "up."}$$




# Capacitors in Series and Parallel

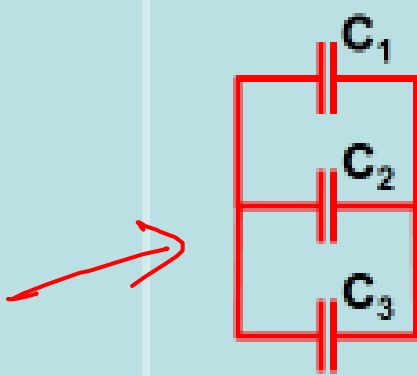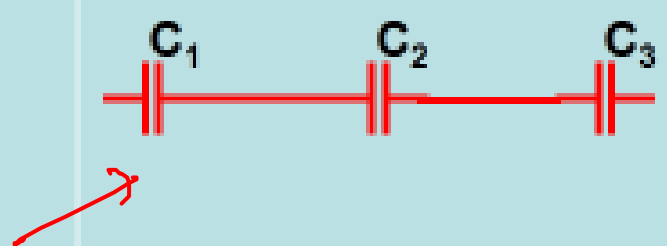	Parallel	Series
		
equivalent capacitance	$C_{eq} = \sum_i C_i$	$\frac{1}{C_{eq}} = \sum_i \frac{1}{C_i}$
charge	Q's add	V's add
voltage	<u>same V</u>	same Q

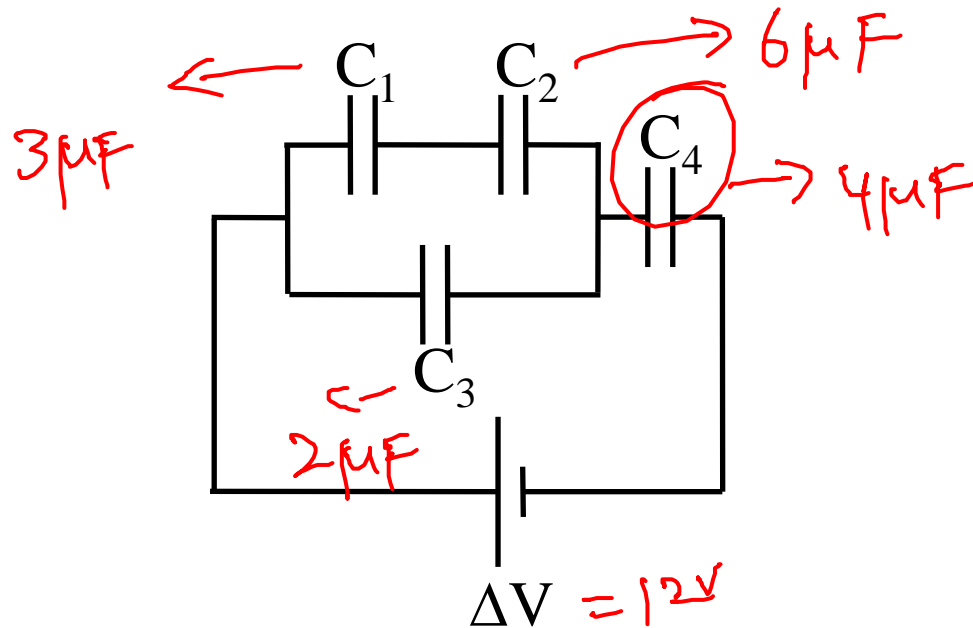**Example:** for the capacitor circuit shown,  $C_1 = 3\mu\text{F}$ ,  $C_2 = 6\mu\text{F}$ ,  $C_3 = 2\mu\text{F}$ , and  $C_4 = 4\mu\text{F}$ . (a) Find the equivalent capacitance. (b) if  $\Delta V = 12\text{ V}$ , find the potential difference across  $C_4$ .



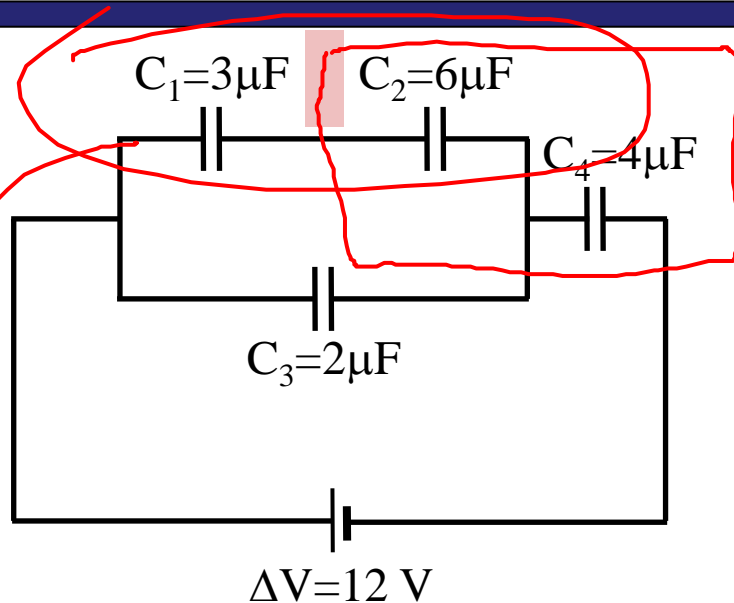(a) Find  $C_{eq}$ . (b) if  $\Delta V = 12 \text{ V}$ , find  $V_4$ .



$C_1$  and  $C_3$  are not in parallel. Make sure you understand why!


$C_2$  and  $C_4$  are not in series. Make sure you understand why!

$C_1$  and  $C_2$  are in series. Make sure you use the correct equation!

$$\frac{1}{C_{12}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{3} + \frac{1}{6} = \frac{2}{6} + \frac{1}{6} = \frac{3}{6} = \frac{1}{2}$$

Don't forget to invert:  $C_{12} = 2 \mu\text{F}$ .

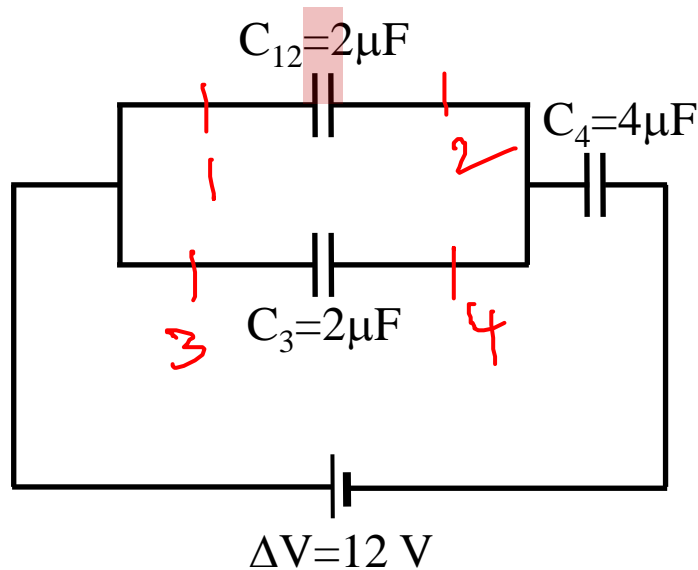(a) Find  $C_{eq}$ . (b) if  $\Delta V = 12 \text{ V}$ , find  $V_4$ .




$C_{12}$  and  $C_4$  are not in series. Make sure you understand why!

$C_{12}$  and  $C_3$  are in parallel. Make sure you use the correct equation!

$$C_{123} = C_{12} + C_3 = 2 + 2 = 4\mu\text{F}$$

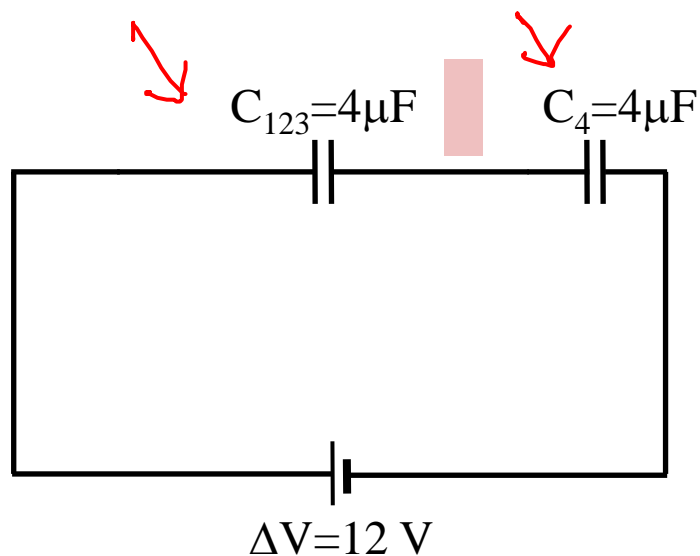(a) Find  $C_{eq}$ . (b) if  $\Delta V = 12 \text{ V}$ , find  $V_4$ .



$C_{123}$  and  $C_4$  are in series. Make sure you understand why! Combined, they make give  $C_{eq}$ .


Make sure you use the correct equation!

$$\frac{1}{C_{eq}} = \frac{1}{C_{123}} + \frac{1}{C_4} = \frac{1}{4} + \frac{1}{4} = \frac{2}{4} = \frac{1}{2}$$

Don't forget to invert:  $C_{eq} = 2 \mu\text{F}$ .




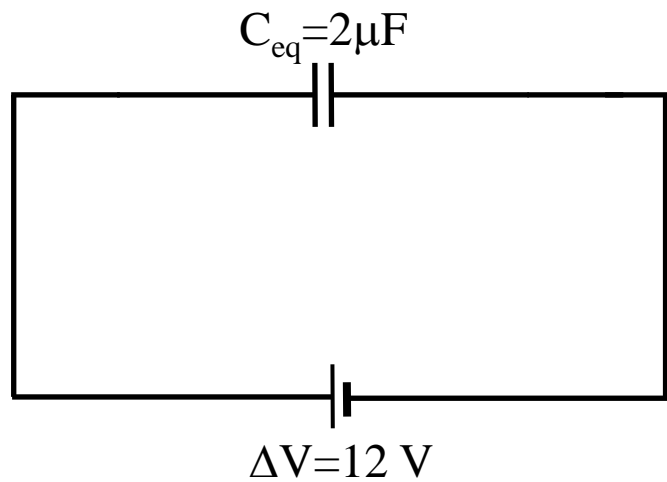(a) Find  $C_{eq}$ . (b) if  $\Delta V = 12 \text{ V}$ , find  $V_4$ .



$$C_{eq} = 2 \mu\text{F}.$$

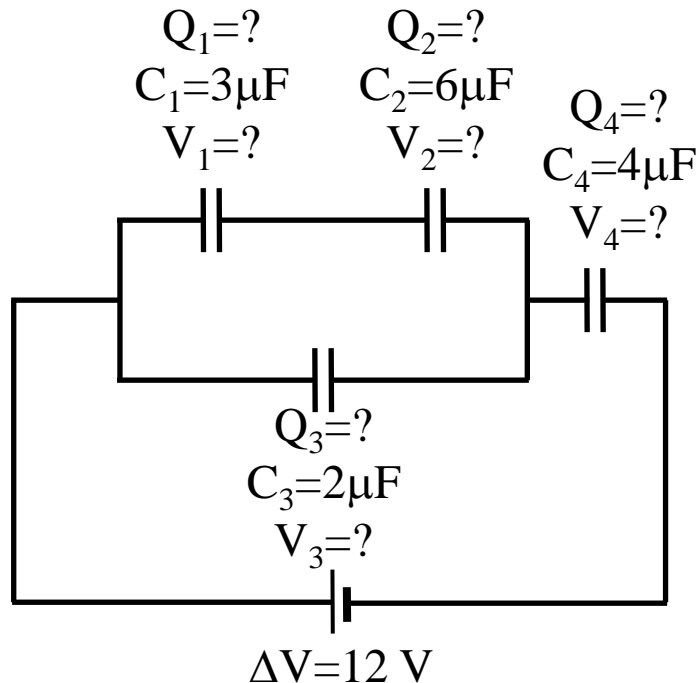(a) Find  $C_{eq}$ . (b) if  $\Delta V = 12 \text{ V}$ , find  $V_4$ .





**Hint:** each capacitor has associated with it a  $Q$ ,  $C$ , and  $V$ . If you don't know what to do next, near each capacitor, write down  $Q =$ ,  $C =$ , and  $V =$ . Next to the  $=$  sign record the known value or a "?" if you don't know the value. As soon as you know any two of  $Q$ ,  $C$ , and  $V$ , you can determine the third. This technique often provides visual clues about what to do next.

We know  $C_4$  and want to find  $V_4$ . If we know  $Q_4$  we can calculate  $V_4$ . Maybe that is a good way to proceed.



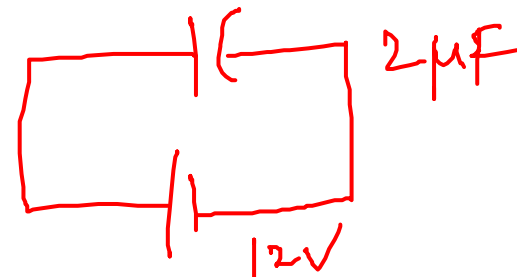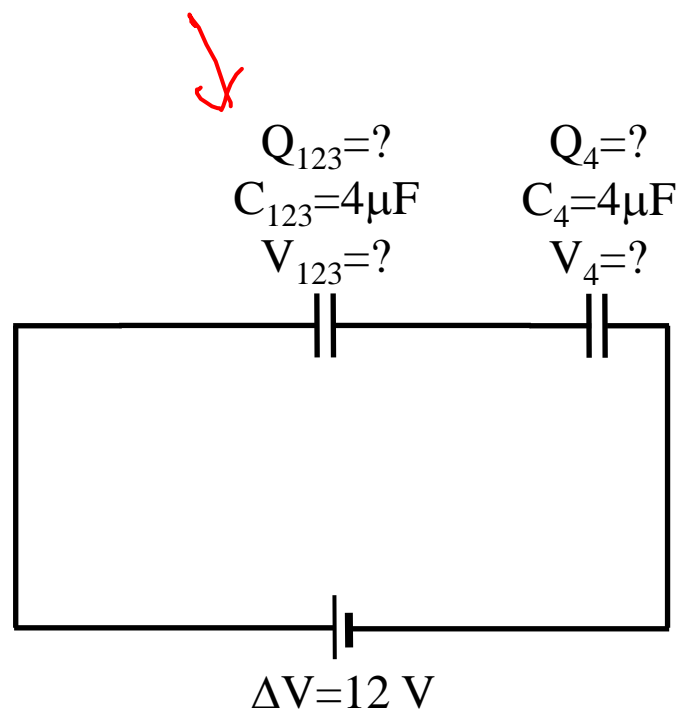(a) Find  $C_{eq}$ . (b) if  $\Delta V = 12 \text{ V}$ , find  $V_4$ .



$C_4$  is in series with  $C_{123}$  and together they form  $C_{eq}$ .

Therefore  $Q_4 = Q_{123} = Q_{eq}$ .

$$Q_{eq} = C_{eq} \Delta V = (2)(12) = \underline{24\mu\text{C}} = \underline{Q_4}$$

$$C = \frac{Q}{V} \Rightarrow \underline{V} = \frac{Q}{C} \Rightarrow V_4 = \frac{Q_4}{C_4} = \frac{24}{4} = \underline{6\text{V}}$$


If you have to calculate the capacitance of a concentric spherical capacitor of charge  $Q$ ...

In between the spheres (Gauss' Law)

$$E = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$|\Delta V| = \frac{Q}{4\pi\epsilon_0} \int_a^b \frac{dr}{r^2} = \frac{Q}{4\pi\epsilon_0} \left[ \frac{1}{a} - \frac{1}{b} \right]$$

$$C = \frac{Q}{|\Delta V|} = \frac{4\pi\epsilon_0}{\left[ \frac{1}{a} - \frac{1}{b} \right]}$$

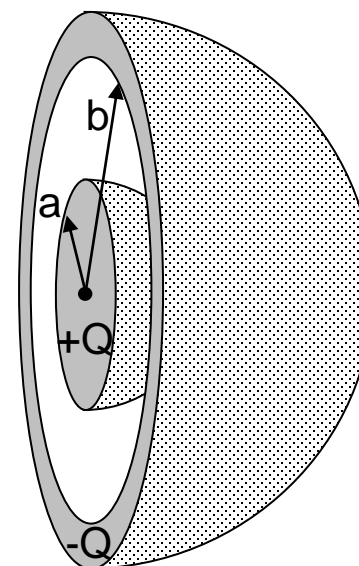

You need to do this derivation **if** you have a problem on spherical capacitors!

# Energy Stored in Electrostatic Field of Capacitance

- The electrostatic field of the charge stored in the dielectric has electric energy supplied by the voltage source that charges C.
- Energy =  $\epsilon = \frac{1}{2} CV^2$  (joules)
  - ✓ C = capacitance (farads)
  - ✓ V = voltage across the capacitor
  - ✓  $\epsilon$  = electric energy (joules)
- Stored energy is the reason why a charged capacitor can produce electric shock even when it is not connected into a circuit.

# Problem

- A parallel plate capacitor with a plate of  $0.25 \text{ m}^2$  and a plate separation of  $6.00 \text{ mm}$  is connected with  $12 \text{ V}$  source. Find:
  - (a) Charge on the capacitor
  - (b) Energy stored in the capacitor
  - (c) Potential difference across the capacitor is reduce to half, explain what will happen to charge on the capacitor and its stored energy

$$C = \frac{\epsilon_0 A}{d}$$

$$U_C = \frac{1}{2} CV^2$$



$$\begin{aligned} \text{(a)} \quad C &= \frac{\epsilon_0 A}{d} \\ &= \frac{(8.854 \times 10^{-12})(0.25 \text{ m}^2)}{0.006 \text{ m}} \\ &= 36.9 \times 10^{-9} \text{ F} \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad U_c &= \frac{1}{2} CV^2 \\ &= \frac{1}{2} (36.9 \times 10^{-9} \text{ F})(12 \text{ V})^2 \\ &= 2.66 \times 10^{-6} \text{ J} \end{aligned}$$

$\text{(c)}$       Since  $Q = CV$ , it halves.  
Since  $UC = \frac{1}{2} CV^2$ , it doubles.

*Synthesis*

# Problem

- *Given some capacitors of  $0.1 \mu\text{F}$  capable of withstanding  $15\text{V}$ . Calculate the number of capacitors needed if it is desired to obtain a capacitance of  $0.1 \mu\text{F}$  for use in a circuit involving  $60 \text{ V}$ .*

# Problem

- *Given some capacitors of  $0.1 \mu\text{F}$  capable of withstanding  $15\text{V}$ . Calculate the number of capacitors needed if it is desired to obtain a capacitance of  $0.1 \mu\text{F}$  for use in a circuit involving  $60 \text{ V}$ .*

# Summary

Capacitors → Electrostatics

\_\_\_\_\_

→ Definition

→ Equations

→ Series / parallel

→ Energy

/ synthesis ?  
↑