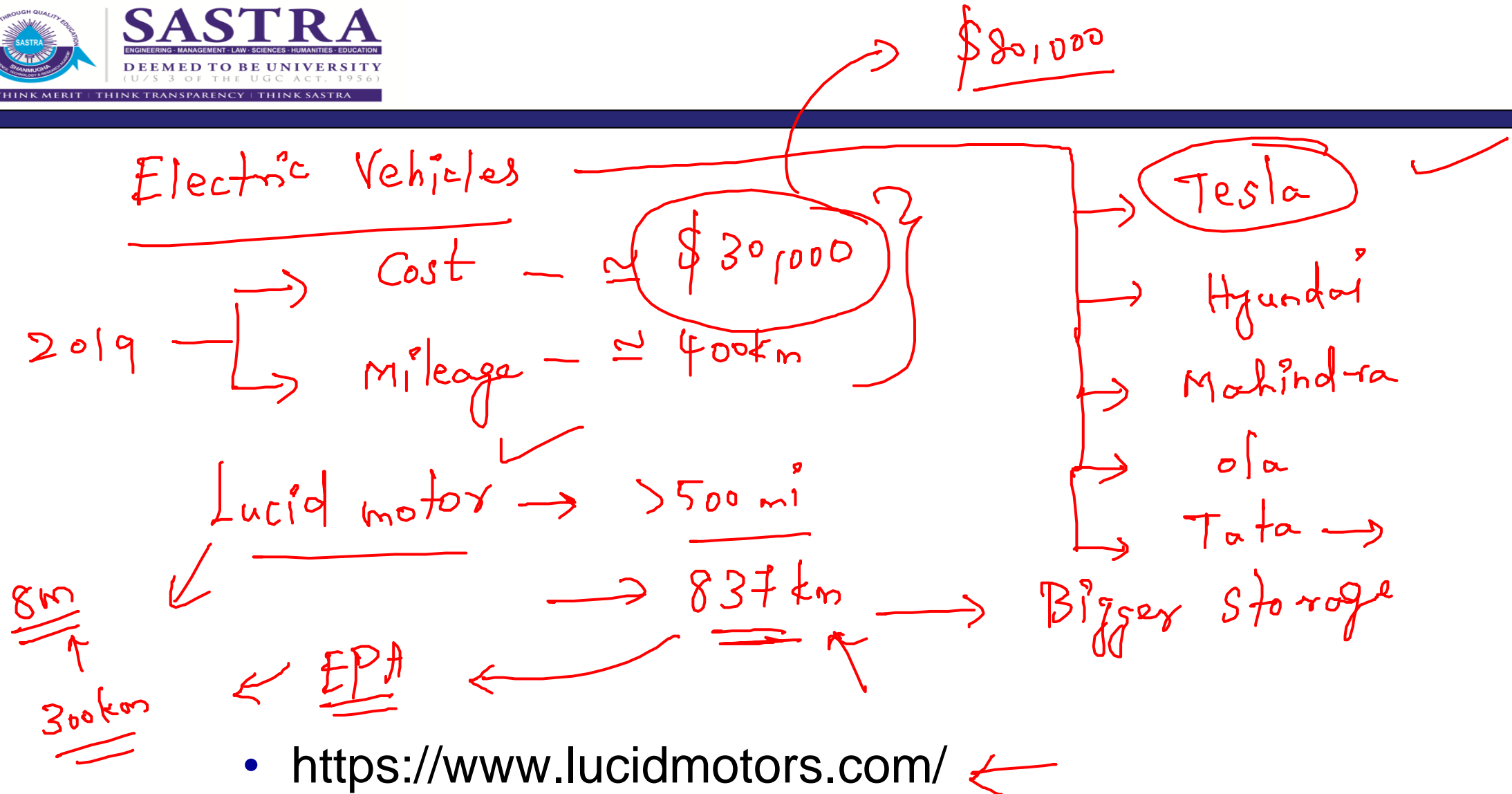


# Unit - II

## 2.3 Mesh Analysis

**Dr.Santhosh.T.K.**



$V$   
 $I$

## Syllabus

Tool chest

- Source
- ohm's
- KVL, KCL
- Mesh Analysis.

### UNIT – II


**14 Periods**

**DC Circuit Analysis:** Voltage source and current sources, ideal and practical, Kirchhoff's laws and applications to network solutions using mesh analysis, - Simplifications of networks using series- parallel, Star/Delta transformation, DC circuits-Current-voltage relations of electric network by mathematical equations to analyse the network (Superposition theorem, Thevenin's theorem, Maximum Power Transfer theorem), Transient analysis of R-L, R-C and R-L-C Circuits.

**AC Steady-state Analysis:** AC waveform definitions - Form factor - Peak factor - study of R-L - R-C -RLC series circuit - R-L-C parallel circuit - phasor representation in polar and rectangular form - concept of impedance - admittance - active - reactive - apparent and complex power - power factor, Resonance in R-L-C circuits - 3 phase balanced AC Circuits
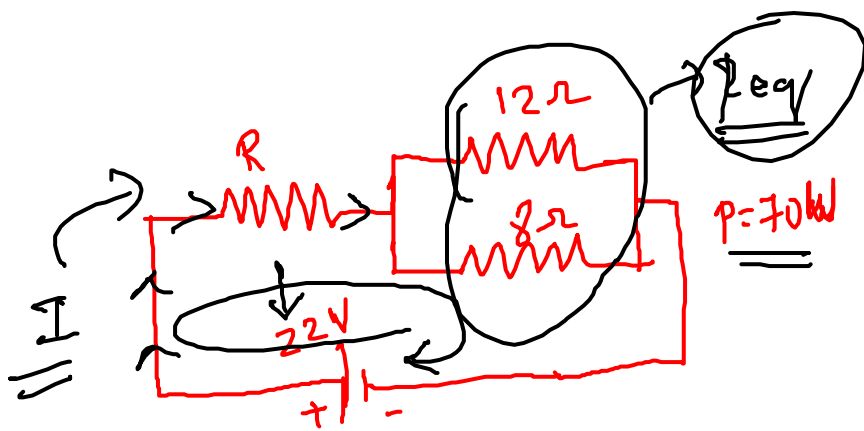
## Exercise - I

- A resistance  $R$  is connected in series with a parallel circuit comprising two resistor  $12\ \Omega$  and  $8\ \Omega$  respectively. The total power dissipated in the circuit is  $70\ \text{W}$ . When the applied voltage is  $22\ \text{volts}$ . Calculate the value of  $R$ .



$$P = V \cdot I$$

$$I = P/V = \frac{70}{22} = 3.18\ \text{A}$$

$$R_{eq} = 12 // 8$$

$$R_{eq} = 4.8\ \Omega$$

$$V_{eq} = I R_{eq} \\ = 3.18 \times 4.8$$

$$V_{eq} = 15.26\ (\text{V})$$

KVL

$$+22 - V_R - V_{eq} = 0$$


$$V_R = 6.73\ (\text{V})$$

$$R = \frac{V}{I}$$

$$R = 2.12\ \Omega$$
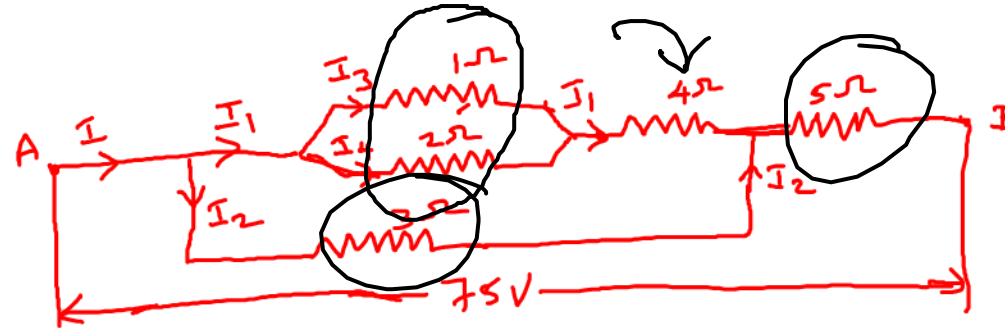
## Practice Problem

- Determine the effective resistance of the series-parallel combination shown in the figure. Also, find the current, voltage and power dissipated in each of the resistor in the given circuit.



$$R_{eq} = 157/23 \Omega$$

$$I = 10.98 A$$

$$I_1 = 4.3 A$$


$$I_2 = 6.78 A$$

$$I_3 = 2.86 A$$

$$I_4 = 1.43 A$$
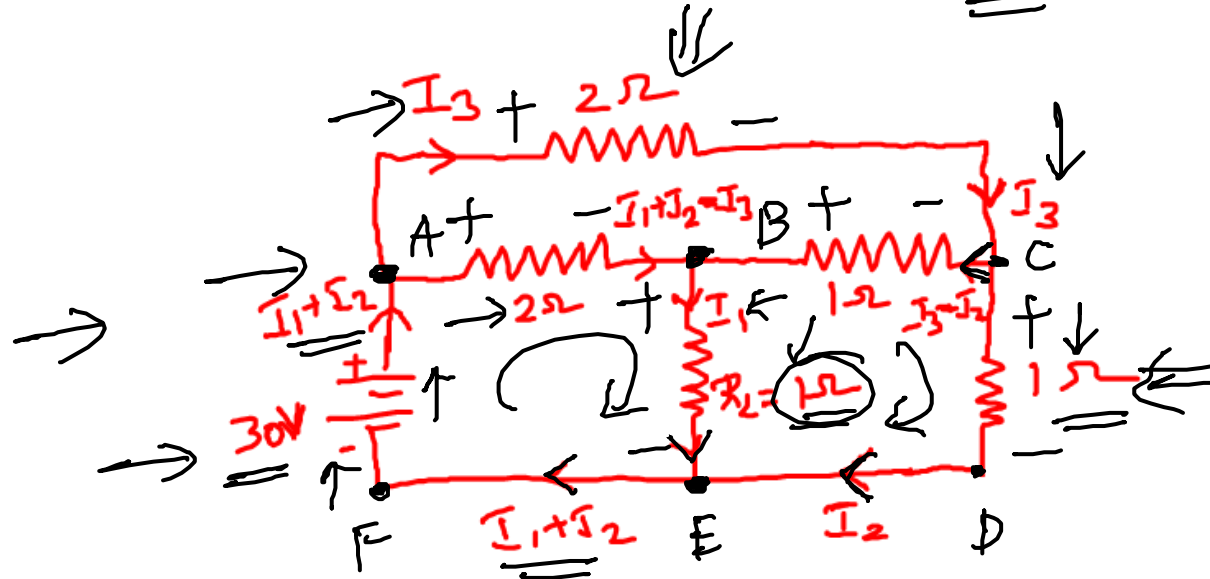
## Practice Problem

Find the load current in the given circuit (Use KVL).



Possible Loops:

$ABEFA$   
 $BCDEB$   
 $ACBA$

Loop 2      KVL

$$+30 - (I_1 + I_2 - I_3)2 - I_1 \cdot 1 = 0$$

Loop II (B C D E B)

$$-(-(I_3 - I_2) \cdot 1) - 1 \cdot I_2 + (-I_1 \cdot 1) = 0$$


Loop III (ACBA)

$$- 2I_3 + (I_3 - I_2) + -(I_1 + I_2 - I_3) \times 2 = 0$$

$\begin{matrix} \text{---} \\ \text{---} \\ \text{---} \end{matrix} \left. \begin{matrix} I_1 = V_L \\ I_2 = \end{matrix} \right\} 10V \quad I_3 = \left. \begin{matrix} \end{matrix} \right\} \rightarrow \underline{10A}$
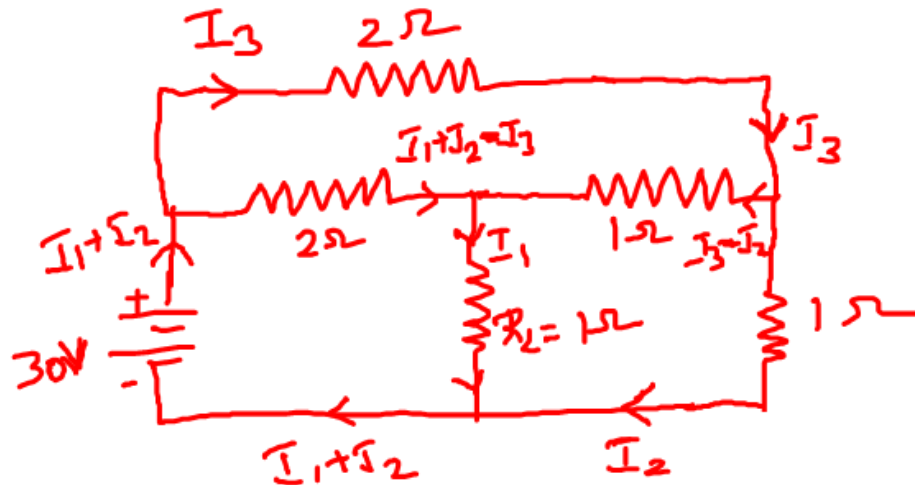
## Practice Problem

Find the load current in the given circuit (Use KVL).



$$V_L = 10\text{ V}$$

# Mesh/Loop Analysis

- Loop analysis is developed by applying KVL around loops in the circuit
- Loop (mesh) analysis results in a system of linear equations which must be solved for unknown currents

More of unknown


Loop →


Mesh →



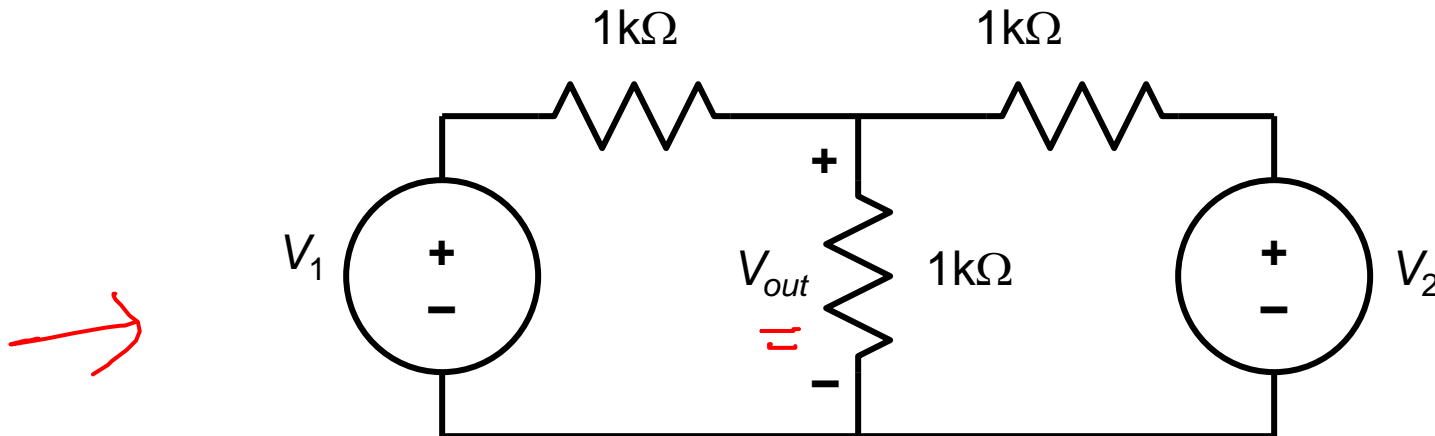
# Summing Circuit

- The output voltage  $V$  of this circuit is proportional to the **sum** of the two input voltages  $V_1$  and  $V_2$




1. **Identify mesh (loops).** 
2. Assign a current to each mesh.
3. Apply KVL around each loop to get an equation in terms of the loop currents.
4. Solve the resulting system of linear equations for the mesh/loop currents.

# 1. Identifying the Meshes

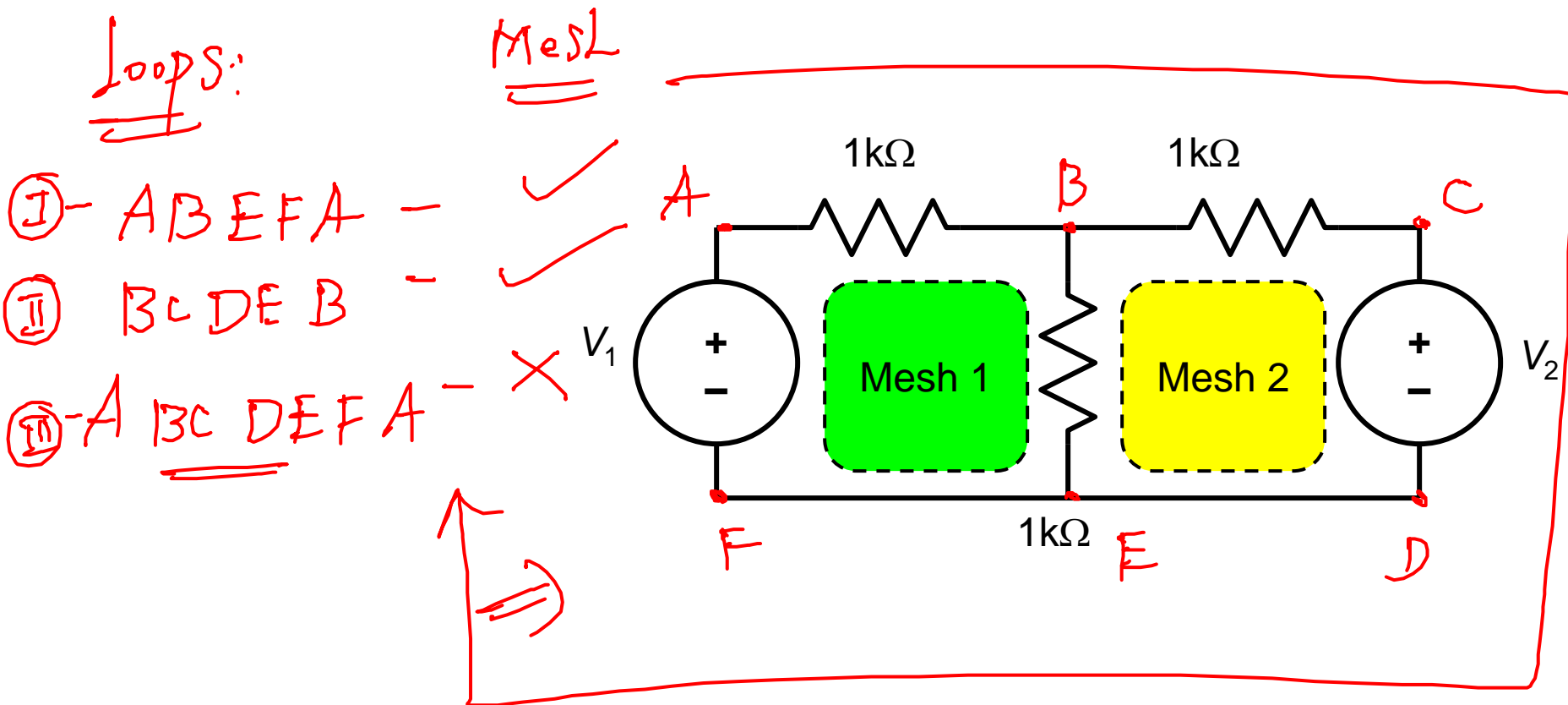

1. Identify mesh (loops).
- 2. Assign a current to each mesh.**
3. Apply KVL around each loop to get an equation in terms of the loop currents.
4. Solve the resulting system of linear equations for the mesh/loop currents.

## 2. Assigning Mesh Currents

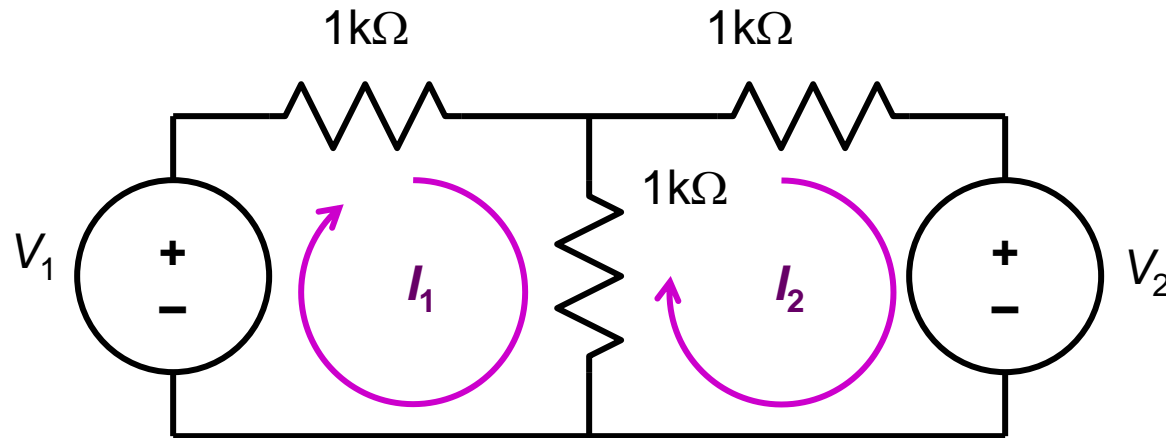


Convention  $\rightarrow$  Assume clockwise currents


# Steps of Mesh Analysis

1. Identify mesh (loops).
2. Assign a current to each mesh.
- 3. Apply KVL around each loop to get an equation in terms of the loop currents.**
4. Solve the resulting system of linear equations for the mesh/loop currents.

# Voltages from Mesh Currents

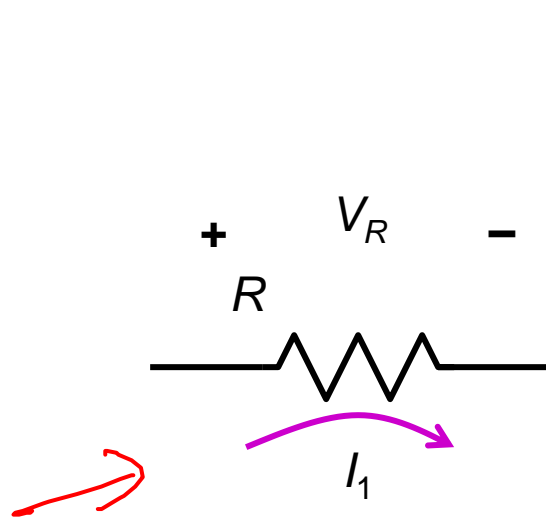

$$\underline{V_R} = \underline{I_1} R$$

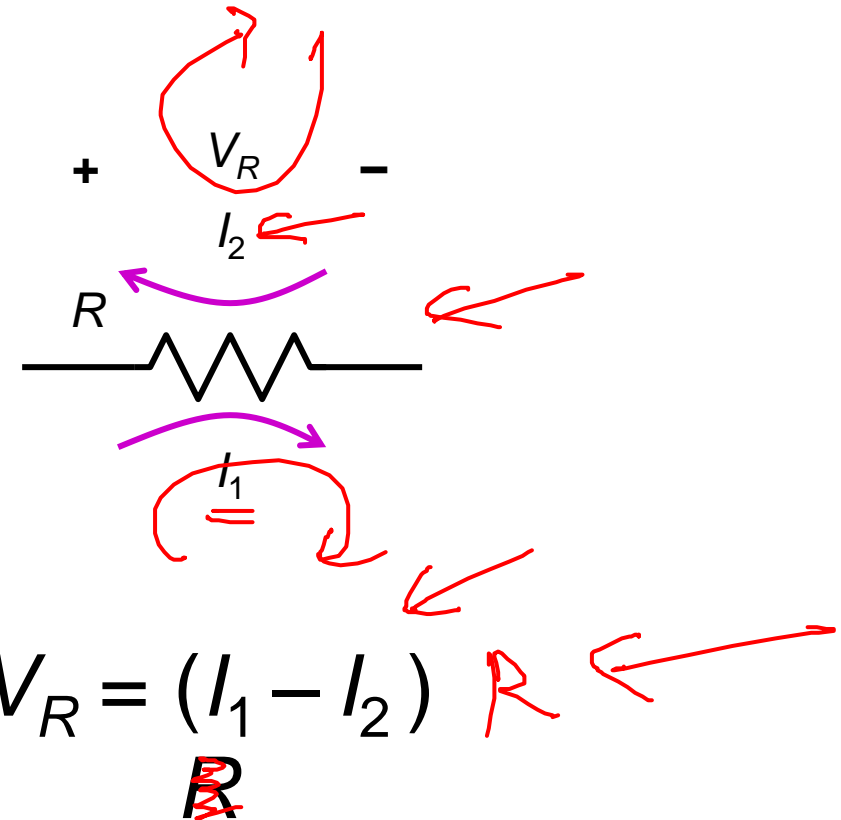


$$V_R = (I_1 - I_2) \underline{R}$$

$$\left. \begin{array}{l} \text{Mesh I} \rightarrow I_1 - I_2 \\ \text{Mesh II} \rightarrow I_2 - I_1 \end{array} \right\}$$

### 3. KVL Around Mesh 1

$$+V_1 - I_1 \cdot 1k - (I_1 - I_2) 1k = 0$$

Resistance drop

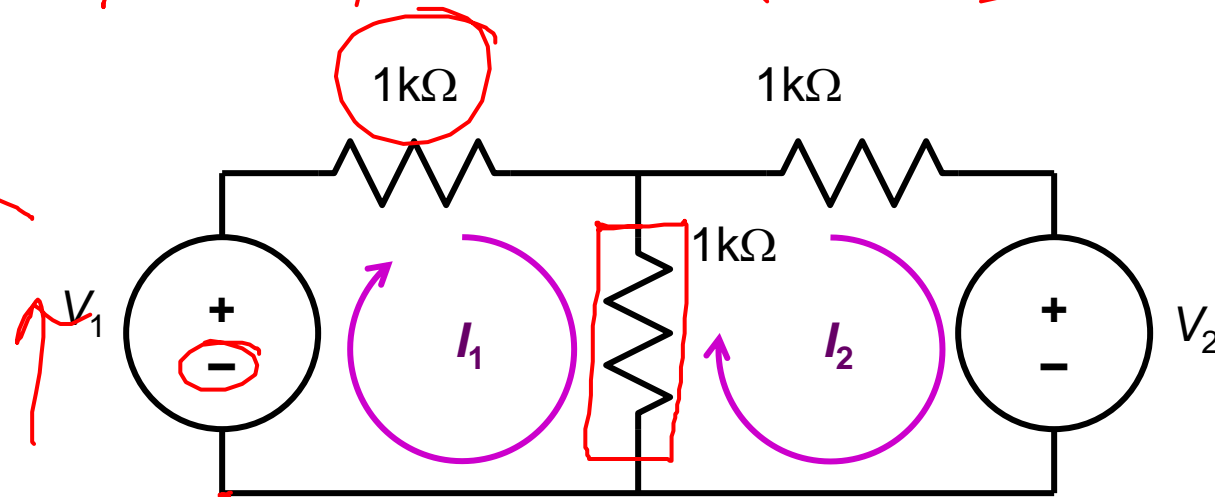

$$+V_1 - I_1 1k\Omega - (I_1 - I_2) 1k\Omega = 0$$


$$I_1 1k\Omega + (I_1 - I_2) 1k\Omega = V_1$$

$$I_1 2k\Omega - I_2 1k\Omega = V_1$$


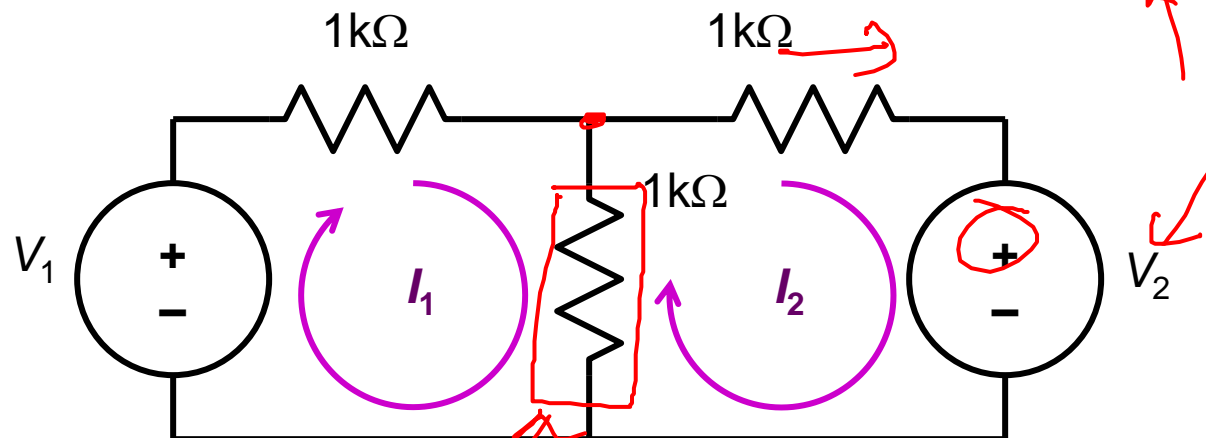
### 3. KVL Around Mesh 2

$$- 1k\Omega \cdot I_2 - V_2 - \underbrace{(I_2 - I_1) 1k}_{\text{Convention}} = 0$$



$$\begin{aligned} -(I_2 - I_1) 1k\Omega - I_2 1k\Omega - V_2 &= 0 \\ (I_2 - I_1) 1k\Omega + I_2 1k\Omega &= -V_2 \\ -I_1 1k\Omega + I_2 2k\Omega &= -V_2 \end{aligned}$$

# Steps of Mesh Analysis

1. Identify mesh (loops).
2. Assign a current to each mesh.
3. Apply KVL around each loop to get an equation in terms of the loop currents.
4. **Solve the resulting system of linear equations for the mesh/loop currents.**

## Exercise

$$V_1 = 7V$$

$$V_2 = 4V$$

$$\begin{array}{l} I_1 = ? \\ I_2 = ? \end{array}$$

# Summary

